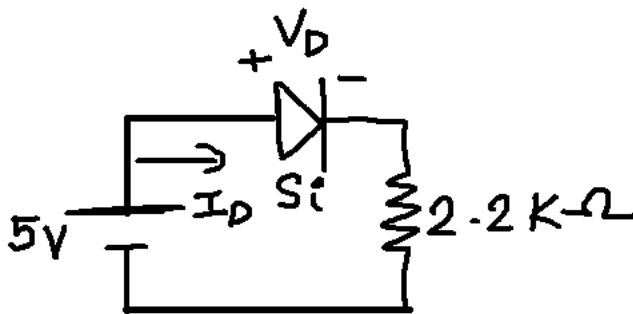



EDC-1 SEM III CBCS (SUBJECT CODE: ELX302) ELECTRONICS ENGINEERING

SAMPLE QUESTIONS (EACH QUESTION CARRIES 2 MARKS)

1. What are the application of PN junction diode
 - a. Switch
 - b. Clipper
 - c. Clamper
 - d. All of the above
2. For the following circuit calculate V_D , I_D , and V_R




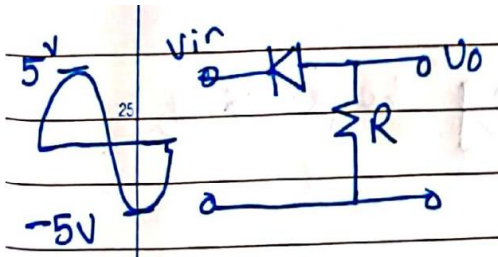- a. $V_D = 0.7V$, $I_D = 1.95mA$, $V_R = 4.29V$
 - b. $V_D = 0.7V$, $I_D = 3mA$, $V_R = 4V$
 - c. $V_D = 0.7V$, $I_D = 5 mA$, $V_R = 4V$
 - d. $V_D = 0.7V$, $I_D = 1mA$, $V_R = 4.29V$
3. Identify the following circuit





- a. Shunt positive Clipper
- b. Series positive clipper
- c. Series negative clipper
- d. Shunt negative Clipper

4. Identify the following circuit

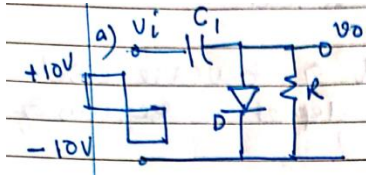


- a. Negative shunt clipper
- b. Positive clamper
- c. Negative clamper
- d. Positive shunt clipper

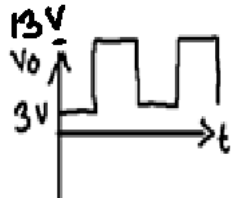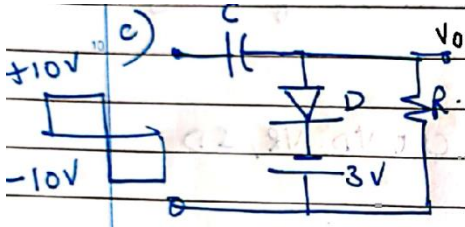
5. What is the output of following circuit?




a.

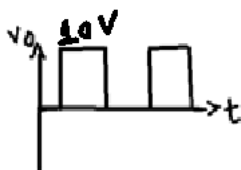


c.

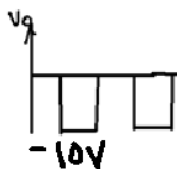


d.

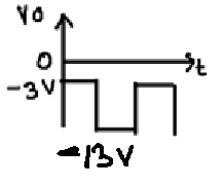

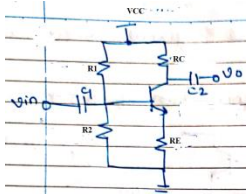6. In CB configuration of BJT input is applied atand output is collected at....
- B and C
 - E and C
 - C and B
 - B and E
7. Identify the type of biasing used in the following circuit diagram




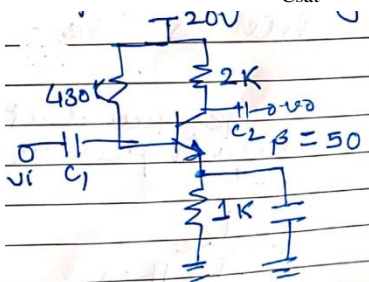- Fixed bias
 - Emitter stabilized bias
 - Feedback bias
 - Voltage divider bias
8. β is the ratio of
- I_B/I_C
 - I_C/I_E
 - I_C/I_B
 - I_E/I_B
9. α is the ratio of
- I_B/I_C
 - I_C/I_E
 - I_C/I_B
 - I_E/I_B
10. What is the value of I_{Csat} for the following circuit



- a. 6.67mA
- b. 0.067 mA
- c. 66.7mA
- d. 0.667 mA

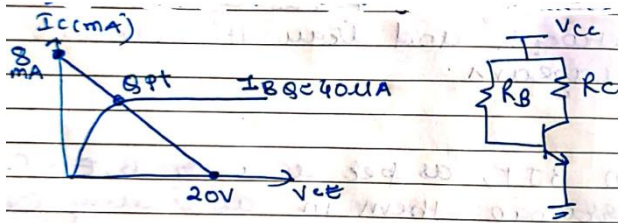11. Determine V_{CC} , R_B and R_C for the following network



- a. 10 V, 200K, 2.4K
- b. 20V, 482.5K, 2.5K
- c. 20V, 267K, 3.2 K
- d. None of the above

12. What is the difference between EMOSFET and DMOSFET?

- a. Channel is present in EMOSFET and absent in DMOSFET
- b. Channel is absent in EMOSFET and present in DMOSFET
- c. Channel is present in both EMOSFET and in DMOSFET
- d. Channel is absent in EMOSFET as well as in DMOSFET

13. Which of the following is Shockley's equation?

- a. $I_D = I_{DSS}(1 - V_{GS}/V_P)^2$
- b. $I_D = I_{DSS}(1 - V_{GS}/V_P)$
- c. $I_D = 2I_{DSS}(1 - V_{GS}/V_P)/|V_P|$
- d. $I_D = 2I_{DSS}(1 - V_{GS}/V_P)^2/|V_P|$

14. What is the current equation for EMOSFET?

- a. $I_D = K_n (V_{GS} - V_{TH})^2$
- b. $I_D = I_{DSS}(1 - V_{GS}/V_P)^2$
- c. $I_D = 2I_{DSS}(1 - V_{GS}/V_P)/|V_P|$
- d. $I_D = 2I_{DSS}(1 - V_{GS}/V_P)^2/|V_P|$

15. Threshold voltage of n Channel EMOSFET is 5V. If 3V is applied at the gate what is the value of drain current?

- a. 1mA
- b. 2mA
- c. 3mA
- a. 0 mA

16. For n channel DMOSET $I_{DSS} = 6\text{mA}$, $V_p = -3\text{V}$, $V_{GS} = -0.8\text{V}$, what is the value of drain current?

- a. 4mA
- b. 4.2mA
- c. 3.22mA
- d. 7mA

17. Transconductance g_m is

- a. Y_{fs}
- b. $1/y_{fs}$
- c. Y_{os}
- d. $1/y_{os}$

18. Drain resistance of FET r_d is given by

- a. Y_{fs}
- b. $1/y_{fs}$
- c. Y_{os}
- d. $1/y_{os}$

19. PIV of full wave bridge rectifier is:

- a. V_m
- b. $V_m/2$
- c. $2V_m$
- d. $3V_m$

20. Ripple factor of half wave rectifier is

- a. 1.21
- b. 2.22
- c. 0.43
- d. 3

21. Output frequency of half wave rectifier is

- a. f
- b. $2f$
- c. $3f$
- d. $4f$

22. Equation of ripple factor of full wave rectifier with filter is given by

- a. $r = 1/4\sqrt{3} fRC$
- b. $r = 1/3\sqrt{3} fRC$
- c. $r = 1/2\sqrt{3} fRC$
- d. $r = 1/2 fRC$

23. Equation of ripple voltage of full wave rectifier with filter is

- a. $V_r(p-p) = V_m / (2fRC)$
- b. $V_r(p-p) = V_m * (2fRC)$
- c. $V_r(p-p) = V_m + (2fRC)$
- d. $V_r(p-p) = V_m - (2fRC)$

24. Efficiency of full wave rectifier with centre tap transformer is

- a. 40.6
- b. 50
- c. 75
- d. 81.2

25. PIV of half wave rectifier is:

- a. V_m
- b. $V_m/2$
- c. $2V_m$
- d. $3V_m$