

University of Mumbai

Examination 2020

Program: BE Electronics Engineering

Curriculum Scheme: Revised 2012 (CBSGS)

Examination: Second Year Semester III


Course Code:EXC304 Course Name: Circuit Theory

Time: 1 hour

Max. Marks: 50

Note:


1. All Questions are compulsory and carry equal marks.
2. Assume suitable data wherever necessary.

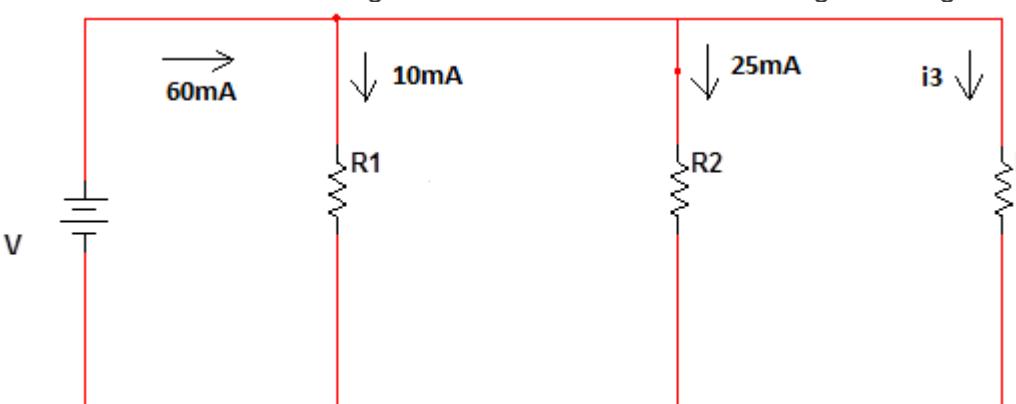Q1.	Which is the condition of symmetry for h parameters
Option A:	$h_{12} = -h_{21}$
Option B:	$h_{11}h_{22} - h_{12}h_{21} = 1$
Option C:	$h_{11}h_{21} - h_{12}h_{22} = 1$
Option D:	$h_{11} = 22$
Q2.	A 25Ω resistor has a voltage of $150 \sin 377 t$. Find the corresponding power.
Option A:	$900 \sin^2 337 t$
Option B:	$90 \sin^2 337 t$
Option C:	$900 \sin^2 377 t$
Option D:	$9 \sin^2 337 t$
Q3.	Determine the current through the resistor R_3 shown in the figure using KCL
	
Option A:	25mA
Option B:	10mA
Option C:	20mA
Option D:	35mA
Q4.	A circuit is given in the figure below. The Thevenin equivalent as viewed from terminals x and x' is

Option A:	8 V and 6 Ω
Option B:	5 V and 6 Ω
Option C:	5 V and 32 Ω
Option D:	8 V and 32 Ω
Q5.	<p>Which is this function network.</p> <p>(a) RL network (b) RC network (c) LC network (d) RLC network</p>
Option A:	
Option B:	
Option C:	
Option D:	

Q6.

Find z parameters.

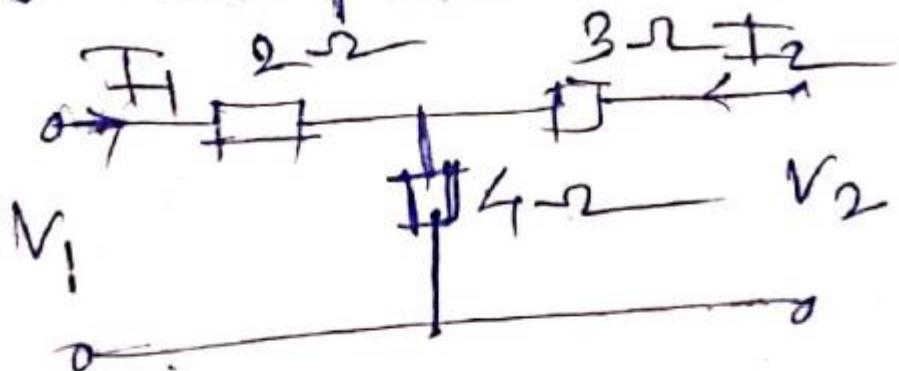

(a) $\begin{bmatrix} 6 & 4 \\ -4 & 7 \end{bmatrix}$

(b) $\begin{bmatrix} 4 & 6 \\ 6 & 7 \end{bmatrix}$

(c) $\begin{bmatrix} 4 & 6 \\ 4 & 6 \end{bmatrix}$

(d) $\begin{bmatrix} 6 & 4 \\ 7 & 4 \end{bmatrix}$

Option A:

Option B:

Option C:

Option D:

Q7. In the following circuit, when $R = 0 \Omega$, the current I_R equals to 10 A. The maximum power will be?

Option A:	50 W
Option B:	100 W
Option C:	200 W
Option D:	400 W
Q8.	. Find the voltage (V) at node 3 in the figure shown below.
Option A:	18
Option B:	20
Option C:	22
Option D:	24
Q9.	The circuit shown in figure has a load equivalent to _____

University of Mumbai

Examination 2020

Option A:	$\frac{4}{3}\Omega$
Option B:	$\frac{8}{3}\Omega$
Option C:	4Ω
Option D:	3Ω
Q10.	The Norton equivalent impedance Z between the nodes P and Q in the following circuit is _____
Option A:	1
Option B:	$1 + s + 1/s$
Option C:	$2 + s + 1/s$
Option D:	$3 + s + 1/s$
Q11.	In the figure given below, the value of Resistance R by Superposition Theorem is _____
Option A:	10
Option B:	20
Option C:	30
Option D:	40
Q12.	The current I in the circuit given below is _____

Option A:	$\frac{1}{4}$
Option B:	$\frac{5}{4}$
Option C:	$\frac{3}{4}$
Option D:	$\frac{1}{2}$
Q13.	The unit step is not defined at $t = ?$
Option A:	0
Option B:	1
Option C:	2
Option D:	3
Q14.	For the network shown in the figure, find the driving point impedance.
Option A:	$(s^2 - 2s + 1)/s$
Option B:	$(s^2 + 2s + 1)/s$
Option C:	$(s^2 - 2s - 1)/s$
Option D:	$(s^2 + 2s - 1)/s$
Q15.	Obtain the transfer function $G_{21}(s)$ in the circuit shown below.
Option A:	$(8s+2)/(8s+1)$
Option B:	$(8s+2)/(8s+2)$
Option C:	$(8s+2)/(8s+3)$
Option D:	$(8s+2)/(8s+4)$

University of Mumbai

Examination 2020

Q16.	Which of the following expression is true in case of open circuit parameters?
Option A:	$V_2 = Z_{21}I_2 + Z_{22} I_2$
Option B:	$V_2 = Z_{21}I_1 + Z_{22} I_2$
Option C:	$V_1 = Z_{21}I_2 + Z_{22} I_2$
Option D:	$V_1 = Z_{21}I_1 + Z_{22} I_2$
Q17.	Find the Z – parameter Z_{11} in the circuit shown below.
Option A:	1
Option B:	1.5
Option C:	2
Option D:	2.5
Q18.	Which of the following expression is true in case of short circuit parameters?
Option A:	$I_2 = Y_{21}I_1 + Y_{22} I_2$
Option B:	$V_2 = Y_{21}I_1 + Y_{22} V_2$
Option C:	$I_2 = Y_{21}V_1 + Y_{22} V_2$
Option D:	$I_2 = Y_{21}V_1 + Y_{22} I_2$
Q19.	.In the circuit shown below, find the transmission parameter A.
Option A:	$6/5$
Option B:	$5/6$
Option C:	$\frac{3}{4}$
Option D:	$4/3$
Q20.	The hybrid parameter h_{21} is called?
Option A:	open circuit output admittance
Option B:	open circuit reverse voltage gain
Option C:	short circuit forward current gain
Option D:	short circuit input impedance
Q21.	For the given information $Z_{11} = 3$, $Z_{12} = 1$, $Z_{21} = 2$, $Z_{22} = 1$. Find the value of Y_{11} .
Option A:	1

University of Mumbai

Examination 2020

Option B:	-1
Option C:	2
Option D:	-2
Q22.	The relation between Z_{22} and Y parameters is?
Option A:	$Z_{22} = (-Y_{11})/\Delta y$
Option B:	$Z_{22} = Y_{21}/\Delta y$
Option C:	$Z_{22} = (-Y_{21})/\Delta y$
Option D:	$Z_{22} = Y_{11}/\Delta y$
Q23.	The roots of the odd and even parts of a Hurwitz polynomial P (s) lie on _____
Option A:	right half of s plane
Option B:	left half of s-plane
Option C:	on $j\omega$ axis
Option D:	on σ axis
Q24.	If the ratio of the polynomial P (s) and its derivative gives a continued fraction expansion with _____ coefficients, then the polynomial P (s) is Hurwitz.
Option A:	all negative
Option B:	all positive
Option C:	positive or negative
Option D:	positive or negative

Q25.

Which is this function.

$$Z(s) = \frac{(s+1)(s+3)}{s(s+2)}$$

- (a) LC function
- (b) RL function
- (c) RC function
- (d) RLC function

Option A:

Option B:

Option C:

Option D: