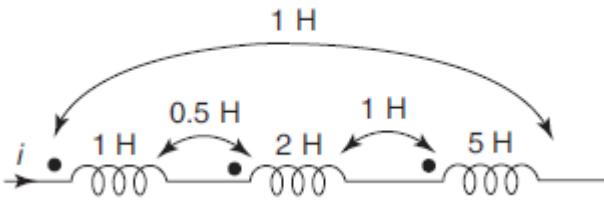
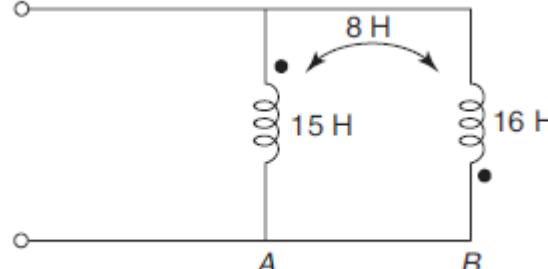


University of Mumbai
Examination 2021 under Cluster 06
(Lead College: Vidyavardhini's College of Engg Tech)
Examination for Direct Second Year Students Commencing from 10th April 2021
Program: Electronics Engineering
Curriculum Scheme: Rev 2019
Examination: SE Semester III (For DSE Students)
Course Code: ELC304 and Course Name: Electrical Network Analysis and Synthesis
Time: 2 hour **Max. Marks: 80**

Q1.	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks
1.	According to Kirchhoff's voltage law, the algebraic sum of all IR drops and e.m.fs. in any closed loop of a network is always Option A: Negative Option B: Positive Option C: Determined by battery e.m.fs. Option D: Zero
2.	For magnetically coupled circuits, $M = K * \sqrt{L_1 * L_2}$, where K represents Option A: Inductance Option B: Coefficient of coupling Option C: Reluctance Option D: Constant
3.	Find the equivalent inductance of the network shown in Fig 
Option A:	13 H
Option B:	8 H
Option C:	10 H
Option D:	9 H
4.	Find the equivalent inductance of the network shown 


Option A:	31 H
Option B:	3.73 H
Option C:	56 H
Option D:	39 H
5.	A capacitor with initial voltage zero, what will be equivalent circuit at t=0+ Option A: Open circuit Option B: Short Circuit Option C: Voltage source Option D: Current source
6.	The EMF induced in a coil due to the changing current in the neighboring coil is called Option A: Self Induced EMF Option B: Differentially Induced EMF Option C: Linearly Induced EMF Option D: Mutually Induced EMF
7.	If all the poles & zeros are lying on negative s-plane (LHS of s-plane) than, the transfer function is Option A: Perfectly Stable Option B: Unstable Option C: Marginally Stable Option D: Infinite
8.	A Inductor with zero initial current flowing, what will be equivalent circuit at t=0+ Option A: Short Circuit Option B: Open Circuit Option C: Voltage Source Option D: Current Source
9.	The s-domain equivalent of voltage source 'V' is written as Option A: V/s Option B: V Option C: s/V Option D: Vs
10.	Which is the condition of symmetry for h parameters Option A: $h_{12} = -h_{21}$ Option B: $h_{11}h_{22}-h_{12}h_{21} = 1$ Option C: $h_{11}h_{21}-h_{12}h_{22} = 1$ Option D: $h_{11} = h_{22}$
11.	Which is the condition of symmetry for ABCD parameters Option A: $AD-BC = 1$ Option B: $B = C$ Option C: $AB - CD = 1$ Option D: $A = D$

12.	The relation between ZOT, Zoc, Zsc is?
Option A:	$Z_{OT} = \sqrt{Z_{oc} Z_{sc}}$
Option B:	$Z_{oc} = \sqrt{(Z_{OT} Z_{sc})}$
Option C:	$Z_{sc} = \sqrt{(Z_{OT} Z_{oc})}$
Option D:	$Z_{oc} = \sqrt{(Z_{OT} Z_{sc})}$
13.	Find the nominal impedance k
	<p>A series circuit diagram showing two inductors of 25 mH each connected in series. A capacitor of 0.2 μF is connected in parallel across the middle point of the series inductors.</p>
Option A:	100 Ω
Option B:	250 Ω
Option C:	500 Ω
Option D:	125 Ω
14.	This is which form of synthesis
	<p>A series circuit diagram showing a 4 H inductor followed by a 1/9 F capacitor in parallel. Below the parallel branch is a T-equivalent circuit consisting of a 15/4 H inductor in series with a 1/15 F capacitor.</p>
Option A:	FOSTER I
Option B:	FOSTER II
Option C:	CAUER I
Option D:	CAUER II
15.	This is which form of synthesis

Option A:	FOSTER I
Option B:	FOSTER II
Option C:	CAUER I
Option D:	CAUER II
16.	<p>This is which type of function</p> $Z(s) = \frac{3(s+2)(s+4)}{s(s+3)}$
Option A:	RC
Option B:	RL
Option C:	LC
Option D:	RLC
17.	<p>This is which type of function</p> $Z(s) = \frac{(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)}$
Option A:	RC
Option B:	RL
Option C:	LC
Option D:	RLC
18.	The number of roots of $s^3 + 5s^2 + 7s + 3 = 0$ in the right half of s-plane is
Option A:	Zero
Option B:	One
Option C:	Two
Option D:	Three
19.	Which are the ABCD Parameter equation
Option A:	$I_1 = AV_2 - BI_2$ $V_1 = CV_2 - DI_2$
Option B:	$I_1 = AV_2 - BI_1$ $V_1 = CV_2 - DI_1$
Option C:	$V_2 = AV_1 - BI_1$ $I_2 = CV_1 - DI_1$
Option D:	$V_1 = AV_2 - BI_2$ $I_1 = CV_2 - DI_2$
20.	For the network in time domain input is $\sin(t)$, then in frequency domain it will become

Option A:	$\frac{1}{s+1}$
Option B:	$\frac{1}{s^2+1}$
Option C:	$\frac{s}{s+1}$
Option D:	$\frac{s}{s^2+1}$

Q2 (20 Marks)	Solve any Four out of Six (5 marks each)
A	In the given network of Fig. the switch is closed at $t = 0$. With zero current in the inductor, find i , di/dt , and d^2i/dt^2 , at $t = 0^+$
B	Find the voltages V_1 and V_2 for the given fig.
C	For the network shown in Fig. determine the current $i(t)$ when the switch is closed at $t = 0$. Assume that initial current in the inductor is zero.
D	Convert Hybrid parameters into ABCD parameters
E	Test whether the polynomial $P(s) = S^4 + S^3 + 5s^2 + 3s + 4$ is Hurwitz
F	Find the characteristic impedance, cut-off frequency and pass band for the network shown in fig.

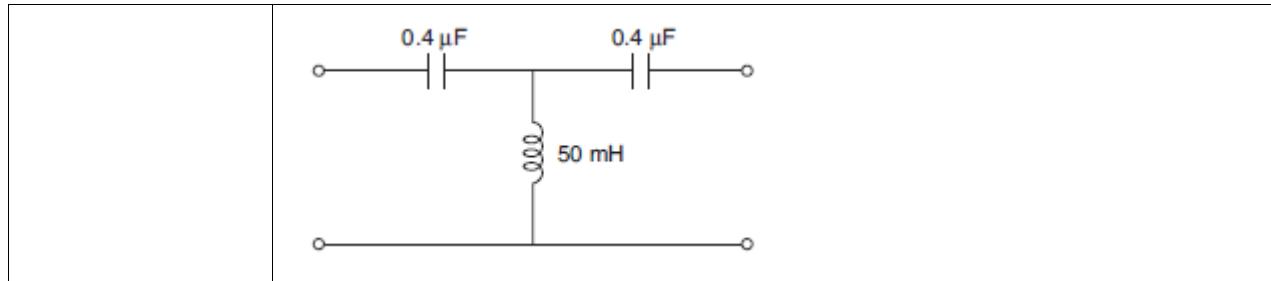

Q3. (20 Marks)	
Q.3 A	Solve any Two (5 marks each)
i.	Write Short note on Filters
ii.	Write the Properties of Positive Real Functions
iii.	Determine the range of values of k so that the polynomial $P(s) = s^3 + 3s^2 + 2s + k$ is Hurwitz.
Q.3 B	Solve any One (10 marks each)
i.	Test whether $F(s) = \frac{2s^3 + 2s^2 + 3s + 2}{s^2 + 1}$ is positive real function.
ii.	Realise the Foster I and Cauer I forms of the impedance function $Z(s) = \frac{(s+1)(s+3)}{s(s+2)}$

University of Mumbai
Examination 2021 under Cluster 06
(Lead College: Vidyavardhini's College of Engg Tech)
Examination for Direct Second Year Students Commencing from 10th April 2021
Program: Electronics Engineering
Curriculum Scheme: Rev 2019
Examination: SE Semester III (For DSE Students)
Course Code: ELC305 and Course Name: Electronics Instruments and Measurement
Time: 2 hour **Max. Marks: 80**
=====

Q1.	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks
1.	Which of the following error can arise as a result of mistake in reading , parallax, improper instrument location and inadequate lighting Option A: Construction error Option B: Transmission Error Option C: Observation Error Option D: Translation Error
2.	Which of the following is static characteristic? Option A: Speed of response Option B: Fidelity Option C: Lag Option D: Resolution
3.	If output characteristics is proportional to Input it is called Option A: Sensitivity Option B: Drift Option C: Linearity Option D: Inverse sensitivity
4.	A simple bridge circuit consists of a network of _____ Option A: 2 resistance arms Option B: 6 resistance arms Option C: 4 resistance arms Option D: 3 resistance arms
5.	Which principle operates a bridge circuit? Option A: Kirchhoff's laws Option B: ampere's rule Option C: partial indication Option D: null indication
6	The analog signal is digitized using _____ Option A: D/A converter Option B: Oscillator

Option C:	A/D converter
Option D:	Rectifier
7	If there is defect in the manufacturing it is
Option A:	Systematic error
Option B:	Gross error
Option C:	Random error
Option D:	Instrument error
8	In a measurement, what is the term associated with magnetism
Option A:	Precision
Option B:	Accuracy
Option C:	Fidelity
Option D:	Hysteresis
9	In function generator, the output waveform of integrator is
Option A:	Sinusoidal
Option B:	Square
Option C:	Triangular
Option D:	Saw-tooth
10	What is not a type of Digital Voltmeter
Option A:	CRT
Option B:	Integrating
Option C:	Ramp Type
Option D:	Successive Approximation
11.	Kelvin's double bridge is used to measure low resistances because
Option A:	It has high sensitivity
Option B:	There is no thermoelectric emf
Option C:	Resistance variation due to temperature
Option D:	Effect of contact and lead resistances is eliminated
12	For very small value of resistances we use
Option A:	Maxwells Bridge
Option B:	Wheatstones bridge
Option C:	Kelvins double bridge
Option D:	Megger
13.	On what Principle does the Q meter operate
Option A:	Series Resonance
Option B:	Parallel Resonance
Option C:	Partial Indication
Option D:	Null Deflection
14.	Wheatstone bridge is a _____
Option A:	A.c. bridge
Option B:	D.c. bridge
Option C:	High voltage bridge
Option D:	Power dissipation bridge

15.	Kelvin's Double bridge works when
Option A:	Ratio of arms is equal
Option B:	Ratio of arms is double
Option C:	When Resistance to be measured is high
Option D:	Ratio of arms is half
16.	Sensitivity is defined as _____
Option A:	The smallest absolute amount of change that can be detected by a measurement.
Option B:	Amount of power detected by instrument
Option C:	Amount of heat generated by resistance
Option D:	Non linearity of Instrument
17.	The desirable static characteristics of a measuring system are
Option A:	Hysteresis
Option B:	Accuracy, sensitivity and reproducibility
Option C:	Drift and dead zone
Option D:	Static error
18.	Which of the following is the dynamic characteristics of an instrument?
Option A:	Reproducibility
Option B:	Sensitivity
Option C:	Dead zone
Option D:	Fidelity
19.	Digital multimeter is used for _____
Option A:	Measuring a.c. And d.c. Current, voltage and resistance
Option B:	Only Measuring a.c. Current and voltage
Option C:	Only Measuring d.c. Current and resistance
Option D:	Only Measuring a.c. Voltage and resistance
20.	Weins Bridge is used for measurement of
Option A:	Temperature
Option B:	Resistance
Option C:	Pressure
Option D:	Capacitance

Q2 (20 Marks)	
Q.2 A	Solve any Two (5 marks each)
i.	Explain the operation of spectrum analyzer.
ii.	Explain need of calibration with suitable example.
iii.	Define and Explain Static Characteristics
Q.2 B	Solve any One (10 marks each)

i.	With a neat diagram, explain the principle of digital Multimeter
ii.	Explain the operation of dual slope and successive approximation type dc voltmeters.

Q3 (20 Marks)	
Q.3 A	Solve any Two (5 marks each)
i.	What is a Super heterodyne wave Analyser
ii.	Explain the operation of peak responding AC voltmeter.
iii.	Explain the operation of Wheatstone bridge.
Q.3 B	Solve any One (10 marks each)
i.	Explain the working of Q meter
ii.	Explain static and dynamic characteristics of an instrument

University of Mumbai

Examinations Commencing from 10th April 2021 to 17th April 2021

Program: **BE Electronics Engineering**

Curriculum Scheme: Rev 2019 'C' Scheme

Examination: SE Semester III

Course Code: **ELC301** and Course Name: **Engineering Mathematics III**

Time: 2 hour

Max. Marks: 80

Note: All Questions are compulsory.

Q1.	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks. 2 marks each
1.	$L[e^{-2t} \cos 3t]$
Option A:	$\frac{s+2}{s^2+4s+13}$
Option B:	$\frac{3}{s^2+4s+13}$
Option C:	$\frac{s-2}{s^2-4s+13}$
Option D:	$\frac{3}{s^2-4s+13}$
2.	$f(x) = x \cos x$ is
Option A:	Even function
Option B:	Odd function
Option C:	Neither even nor odd
Option D:	Both even and odd
3.	Find k such that $f(z) = (x^3 - kxy^2 + 3x^2 - 3y^2) + i(kx^2y - y^3 + 6xy)$ is analytic
Option A:	$K = 3$
Option B:	$K = -3$
Option C:	$K = 0$
Option D:	$K = 2$
4.	Find the characteristic roots of matrix A , Where $A = \begin{bmatrix} -2 & 5 & 4 \\ 5 & 7 & 5 \\ 4 & 5 & -2 \end{bmatrix}$
Option A:	$\lambda = 12, 3, 6$
Option B:	$\lambda = 1, 3, -6$
Option C:	$\lambda = 12, -3, -6$
Option D:	$\lambda = -2, -3, -6$
5.	The function $f(x,y)$ is harmonic if
Option A:	$\frac{\partial^2 f}{\partial x^2} - \frac{\partial^2 f}{\partial y^2} = 0$

Option B:	$\frac{\partial^2 f}{\partial x^2} - \frac{\partial^2 f}{\partial y^2} = 1$
Option C:	$\frac{\partial^2 f}{\partial x^2} + \frac{\partial^2 f}{\partial y^2} = 1$
Option D:	$\frac{\partial^2 f}{\partial x^2} + \frac{\partial^2 f}{\partial y^2} = 0$
6.	Laplace Transform of $\sin^2 t$ is
Option A:	$\frac{1}{2} \left[\frac{1}{s} + \frac{1}{s^2+4} \right]$
Option B:	$\frac{1}{2} \left[\frac{1}{s} - \frac{2}{s^2+4} \right]$
Option C:	$\frac{1}{2} \left[\frac{1}{s} + \frac{s}{s^2+4} \right]$
Option D:	$\frac{1}{2} \left[\frac{1}{s} - \frac{s}{s^2+4} \right]$
7.	The value of Fourier coefficient a_0 in the Fourier expansion of $f(x) = \frac{1}{2}(\pi - x)$ in $(0, 2\pi)$ is
Option A:	0
Option B:	1
Option C:	$\frac{\pi}{4}$
Option D:	$\frac{1}{4\pi}$
8.	$\lambda = 4$ is one of the eigenvalue of $A = \begin{bmatrix} 1 & -3 & 3 \\ 3 & -5 & 3 \\ 6 & -6 & 4 \end{bmatrix}$. The eigenvector corresponding to eigenvalue $\lambda = 4$ is
Option A:	$[1 \ -1 \ 2]'$
Option B:	$[1 \ 1 \ 2]'$
Option C:	$[2 \ -1 \ -1]'$
Option D:	$[2 \ 1 \ -1]'$
9.	If $\text{curl } \bar{F} = 0$, then \bar{F} is called
Option A:	Solenoidal
Option B:	irrotational
Option C:	constant
Option D:	Zero
10.	Find Laplace transform of $f(t) = 3, 0 < t < 1$ $= 0, t \geq 1$
Option A:	$\frac{1 - e^{-s}}{3s}$
Option B:	$\frac{e^{-s} - 1}{3s}$
Option C:	$\frac{1}{s}$
Option D:	$\frac{3(1 - e^{-s})}{s}$
11.	Function $f(x)$ defined in the interval (a, b) can be expressed in Fourier series

Option A:	If $f(x)$ is of exponential order
Option B:	If $f(x)$ is even function
Option C:	If $f(x)$ satisfies Dirichlet's condition
Option D:	If $f(x)$ is odd function
12.	If $A = \begin{bmatrix} 1 & 2 & 0 \\ 0 & -1 & 3 \\ 0 & 0 & 1 \end{bmatrix}$ Find Eigen Values of $A^2 + I$
Option A:	1,-1,1
Option B:	2,2,2
Option C:	1,1,1
Option D:	2,0,2
13.	The function $\frac{1}{z}$ is
Option A:	Analytic at zero
Option B:	Analytic at all points
Option C:	Not analytic at zero
Option D:	Not analytic at all points
14.	If $L[t^{3/2}] = ?$
Option A:	$\frac{3\sqrt{\pi}}{2s^{5/2}}$
Option B:	$\frac{3\sqrt{\pi}}{4s^{5/2}}$
Option C:	$\frac{3\sqrt{\pi}}{4s^{3/2}}$
Option D:	$\frac{3\sqrt{\pi}}{4s^{3/2}}$
15.	If eigen values of matrix A are 2,-2,3 then the value of $ A $ is
:	12
Option B:	3
Option C:	-12
Option D:	0
16.	Find $L^{-1}\left[\frac{s^2+2s+2}{s^3}\right]$
Option A:	$1+t+t^2$
Option B:	$1+t+2t^2$
Option C:	$1+2t+t^2$
Option D:	$1+2t+2t^2$
17.	$L^{-1}\left[\frac{s+1}{(s+1)^2-1}\right]$ is
Option A:	$e^t \cosh t$
Option B:	$e^{-t} \cosh t$
Option C:	$e^t \cos t$
Option D:	$e^{-t} \sinh t$

18.	Orthogonal trajectories of the family of the curves $u=c_1$ is given by
Option A:	$v = c_2$
Option B:	$u + v = c$
Option C:	$u - v = c$
Option D:	$uv = c_2$
19.	$L \left[\int_0^t \int_0^t \sin u \, du \, du \right] = ?$
Option A:	$\frac{1}{s^{2+1}}$
Option B:	$\frac{1}{s(s^2+1)}$
Option C:	$\frac{1}{s^2(s^2+1)}$
Option D:	$\frac{s}{s^2+1}$
20.	What is the divergence of the vector field $\bar{F} = x^2\mathbf{i} + 5y^2\mathbf{z}\mathbf{j} + xyz^2\mathbf{k}$ at the point $(1, 0, -1)$
Option A:	1
Option B:	2
Option C:	3
Option D:	4

Q2.	Solve any Four out of Six	5 marks each
A	Use Laplace Transform to evaluate $\int_0^\infty \frac{e^{-2t}-e^{-3t}}{t} dt$	
B	Find inverse laplace transform of $\log\left(\frac{s+2}{s+3}\right)$	
C	Obtain the fourier series for $f(x) = x^3$ in $(-\pi, \pi)$	
D	Show that the matrix $A = \begin{bmatrix} 4 & 2 & 2 \\ 2 & 4 & 2 \\ 2 & 2 & 4 \end{bmatrix}$ is diagonalizable	
E	Find the orthogonal trajectories of the family of the curves $2x - x^3 + 3xy^2 = c$	
F	Using Green's theorem evaluate $\int_C x^2y \, dx + (y^3) \, dy$ where C is the boundary of the surface enclosed by $y = x, y = x^2$.	

Q3.	Solve any Four out of Six	5 marks each
A	Find $L \left[\int_0^t \frac{e^{-u} \sin 2u}{u} \, du \right]$	
B	Verify Cayley-Hamilton Theorem and hence find inverse of the matrix $\begin{bmatrix} 4 & 6 & 6 \\ 1 & 3 & 2 \\ -1 & -5 & -2 \end{bmatrix}$	
C	Find half range sine series for $f(x) = x - x^2$ in $(0,1)$	
D	Using convolution theorem, Find $L^{-1} \left(\frac{s}{(s^2+4)^2} \right)$	

E	Find the analytic function whose real part is $u = e^x \cos y$
F	Evaluate $\int_C \vec{F} \cdot d\vec{r}$ where, $\vec{F} = (3x^2 + 6y)i - 14yzj + 20xz^2k$ and c is the straight line joining (0,0,0) and (1,1,1)

University of Mumbai
Examination 2021 under Cluster 06
(Lead College: Vidyavardhini's College of Engg Tech)
Examination for Direct Second Year Students Commencing from 10th April 2021
Program: Electronics Engineering
Curriculum Scheme: Rev 2019
Examination: SE Semester III (For DSE Students)
Course Code: ELC302 and Course Name: Electronic Devices and Circuits I
Time: 2 hour **Max. Marks: 80**

Q1.	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks
1.	Fermi energy level for n-type semiconductors lies -----and P type semiconductor lies ----- Option A: Close to conduction band , Close to valence band Option B: Close to conduction band , Close to conduction band Option C: Close to valence band , Close to conduction band Option D: Close to valence band, Close to valence band
2.	In any semiconductor material, the drift current is proportional to Option A: Concentration gradient of charge carriers Option B: Square of applied electric field Option C: Applied electric field Option D: Cube of applied electric field
3.	In fixed bias circuit using an NPN transistor, if $V_{CC} = 12V$, $V_{BE}=0.7V$, Base resistor $R_B= 240 k$ then I_B is Option A: $80 \mu A$ Option B: $47 \mu A$ Option C: $50 \mu A$ Option D: $130 mA$
4.	H parameter model consists of components such as Option A: small signal resistance r_{pi} and a dependent current source gmV_{pi} Option B: input impedance, reverse voltage gain, current gain and output conductance Option C: small signal resistance r_e and a controlled current source Option D: small signal resistance r_{pi} and an independent current source gmV_{pi}
5.	Which Configuration has a high input impedance and low output impedance Option A: Common Collector Configuration Option B: Common Base Configuration Option C: Common Emitter Configuration Option D: Collector Base Configuration
6.	In a bipolar junction transistor (BJT) if $\beta = 100$ & collector current (I_C) is $0.93 mA$ then what is the value of base current (I_B) ? Option A: $9.3 \mu A$ Option B: $0.93 \mu A$

Option C:	93 μ A
Option D:	93 mA
7.	To operate transistor in its forward active / linear mode of operation base emitter junction is ----- and the collector base junction is -----
Option A:	reverse biased, forward biased
Option B:	reverse biased, reverse biased
Option C:	forward biased ,reverse biased
Option D:	forward biased, forward biased
8.	The voltage gain of a common base amplifier is
Option A:	Zero
Option B:	Less than unity
Option C:	Unity
Option D:	Greater than unity
9.	The relation between α and β is
Option A:	$\alpha = (1+\beta)/\beta$
Option B:	$\alpha = \beta/(1+\beta)$
Option C:	$\alpha = \beta/(1-\beta)$
Option D:	$\alpha = (1-\beta)/\beta$
10.	In case of DMOSFET drain current I_D depends upon
Option A:	V_{dd}
Option B:	I_G
Option C:	V_{GS}
Option D:	I_S
11.	For E-MOSFETs, the relationship between output current and controlling voltage is defined by-----.
Option A:	$ID = [(V_{GS} - V_{GS(Th)})]^2$
Option B:	$ID = k [(V_{GS} - V_{SB})]^2$
Option C:	$ID = k [(V_{GS} - V_{DS})]^2$
Option D:	$ID = k [(V_{GS} - V_{GS(Th)})]^2$
12.	The N channel connecting two N regions is absent in
Option A:	N channel DMOSFET
Option B:	N channel EMOSFET
Option C:	P channel DMOSFET
Option D:	P channel EMOSFET
13.	The biasing method used for EMOSFET are voltage divider biasing circuit and---
Option A:	self bias circuit
Option B:	fixed bias
Option C:	collector to base bias circuit
Option D:	feedback biasing circuit
14.	The input impedance of the MOSFET is very high .Give reason

Option A:	The SiO_2 layer is present between gate terminal and channel.
Option B:	Metallic contacts are used for connecting the Drain, gate and source terminals
Option C:	A P type semiconductor is used as a substrate.
Option D:	A N type semiconductor is used as a substrate.
15.	A common drain amplifier has voltage gain _____
Option A:	Slightly less than 1.
Option B:	Greater than 1
Option C:	Infinite
Option D:	Zero
16.	Input signal of common source amplifier is applied to _____
Option A:	Source terminal
Option B:	Gate terminal
Option C:	Drain terminal
Option D:	Substrate terminal
17.	Phase difference between input and output of a source follower circuit is
Option A:	0 degree
Option B:	90 degrees
Option C:	180 degrees
Option D:	45 degrees
18.	For the CS amplifier circuit calculate voltage gain A_v if $g_m = 200 \text{ micro A/V}$ and $R_D = 14\text{K}\Omega$
Option A:	-2.8
Option B:	2.8
Option C:	4.8
Option D:	-4.8
19.	Reactance of capacitor is given by
Option A:	$X_C = 1/2 \pi f C$
Option B:	$X_C = 1/2 \pi R C$
Option C:	$X_C = 1 / 2 \pi L C$
Option D:	$X_C = 1 / 2 \pi R L$
20.	In the design steps for RC coupled CE amplifiers, the voltage drop across emitter resistor R_E should be ----- as compared to base emitter voltage of transistor
Option A:	lower
Option B:	higher
Option C:	same
Option D:	Zero

Q2. (20 Marks)	
Q.2 A)	Solve any two out of three (5 marks each)
i.	Draw Energy band diagram of PN junction diode under Forward biased, Reverse biased and Zero biased.
ii.	Compare CE, CB, CC Configurations of BJT.
iii.	Explain hybrid π model of BJT.
Q2. B)	Solve any One Question out of two. (10 marks each)
i.	Design a single stage RC Coupled CE amplifier using transistor with given specifications as $ Av =70$, $V_o \text{ rms}=4.5V$, $F_L=10 \text{ Hz}$, $V_{CE(\text{SAT})}=1V$, $h_{FE}= 180$, $h_{IE}=2.7K\Omega$ and $S<8$.
ii.	Draw the neat diagram of voltage divider biased CS MOSFET amplifier and source resistance bypass and derive the expression for the voltage gain.

Q3). (20 Marks)	Solve any Two Questions out of Three (10 marks each)
A	<p style="text-align: center;">Fig.1</p> <p>For the voltage divider bias circuit shown in Fig. 1 using N-channel E-MOSFET, $V_{DD}=40V$, $V_{GS(TH)}=5V$, $I_D(ON)= 3 \text{ mA}$ and $V_{GS(ON)}=10V$. Calculate Q - point where $Q = [V_{DSQ}, I_{DQ}]$.</p>

B

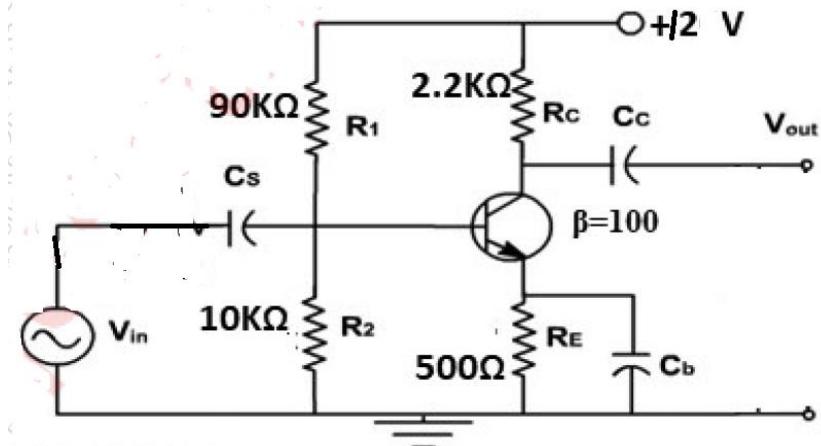


Fig. 2

$R_1=90\text{K}\Omega$, $R_2=10\text{K}\Omega$, $V_{cc}=12\text{V}$, $\beta=100$, $V_{BE}=0.7\text{V}$, $R_c=2.2\text{K}\Omega$, $R_E=500\Omega$

Find out voltage gain A_v , input impedance R_i and output impedance R_o for the given circuit in Fig. 2

C

Design a single stage RC Coupled CE amplifier using transistor with following specifications.

$h_{fe}=220$, $h_{ie}=2.7\text{K}\Omega$, $|A_v|=180$, $S=10$, $V_o=3\text{V}$, $V_{cc}=18\text{V}$, $F_L=20\text{Hz}$, $V_{CE(SAT)}=1\text{V}$

University of Mumbai
Examination 2021 under Cluster 06
(Lead College: Vidyavardhini's College of Engg Tech)
Examination for Direct Second Year Students Commencing from 10th April 2021
Program: Electronics Engineering
Curriculum Scheme: Rev 2019
Examination: SE Semester III (For DSE Students)
Course Code: ELC303 and Course Name: Digital Logic Circuits
Time: 2 hour **Max. Marks: 80**

Q1.	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks
1.	Convert Decimal(105) ₁₀ to Binary
Option A:	(101001) ₂
Option B:	(1101001) ₂
Option C:	(1110101) ₂
Option D:	(1001011) ₂
2.	In Hamming code, which expression will help you to find out the number of parity bits.
Option A:	$2^P \geq P+M+1$
Option B:	$2^P \leq P+M+1$
Option C:	$2^P = P+M-1$
Option D:	$2^P \leq P+M-1$
3.	What is the reflected binary code of (100101) ₂ .
Option A:	111000
Option B:	101010
Option C:	101111
Option D:	110111
4.	A multiplexer with 3 select lines is a
Option A:	4:1 multiplexer
Option B:	8:1 multiplexer
Option C:	16:1 multiplexer
Option D:	32:1 multiplexer
5.	IC 74138 is a
Option A:	3:8 line decoder
Option B:	1:8 line decoder
Option C:	4:8 line decoder
Option D:	any lines to 8 line decoder
6.	Which of the following ICs can be used as a comparator?
Option A:	IC7408
Option B:	IC7400

Option C:	IC7485
Option D:	IC7420
7.	In which type of machine the output depends on the present state and external input.
Option A:	Mealy machine
Option B:	Sequential asynchronous machine
Option C:	Asynchronous machine
Option D:	Moore machine
8.	IC 7492 is a
Option A:	MOD 12 Asynchronous counter
Option B:	MOD 12 Synchronous counter
Option C:	MOD 16 Asynchronous counter
Option D:	MOD 16 Synchronous counter
9.	Which of the following is a decade counter?
Option A:	IC 7493
Option B:	IC 7490
Option C:	IC 7491
Option D:	IC 7492
10.	Which one of the following methods can be used for state reduction?
Option A:	K-Maps
Option B:	Implication Chart method
Option C:	Truth Table
Option D:	Quine Mcclusky method
11.	Which of the given logic family dissipates minimum power
Option A:	TTL
Option B:	CMOS
Option C:	DTL
Option D:	ECL
12.	IC 74194 is a
Option A:	Ring counter
Option B:	4-bit bidirectional universal shift register
Option C:	Unidirectional shift register
Option D:	4-bit register
13.	What does FPGA stand for
Option A:	Field Programming Gate Array
Option B:	Field Programmable Gate Array
Option C:	First Program Gate Array
Option D:	First Programmable Gate Array
14.	Programmable Array Logic has
Option A:	a programmable AND and fixed OR array
Option B:	a programmable AND and a programmable OR array

Option C:	only a programmable AND array
Option D:	only a programmable OR array
15.	The number of similar gates which can be driven by a gate is called as _____
Option A:	Power dissipation
Option B:	Noise margin
Option C:	Fan-out
Option D:	Speed
16.	A CPLD device consist of
Option A:	PAL-Like Blocks, I/O blocks, and a set of interconnection wires
Option B:	PLA-Like Blocks and I/O blocks
Option C:	FPGAs
Option D:	Only interconnecting wires
17.	Which type of modeling style is not used in verilog hardware description language
Option A:	Structural
Option B:	Datatype
Option C:	Behavioral
Option D:	Data Flow
18.	_____ is a net data type used in Verilog.
Option A:	reg
Option B:	integer
Option C:	real
Option D:	wire
19.	Register data type in Verilog HDL is denoted as
Option A:	reg
Option B:	register
Option C:	RG
Option D:	wire
20.	Comment lines in Verilog HDL is denoted by
Option A:	//
Option B:	\
Option C:	\\\
Option D:	*

Q2 (20 Marks)	
A	Solve any Two 5 marks each
i.	Explain with neat diagrams working of IC7483
ii.	State the differences between mealy and moore machine.
iii.	Write a short note on Complex Programmable Logic Devices.
B	Solve any One 10 marks each

i.	Design a MOD-6 counter using IC7490.
ii.	Write a program using Verilog HDL to implement a 8:1 multiplexer.
Q3 (20 Marks)	
A	Solve any Two 5 marks each
i.	Explain with suitable diagrams working of IC74163.
ii.	Write a program using Verilog HDL for implementing a half adder.
iii.	Explain in brief about the interfacing of CMOS to TTL ICs.
B	Solve any One 10 marks each
i.	Write a short note on carry look ahead adder.
ii.	Analyze the given state machine and draw the state diagram.

