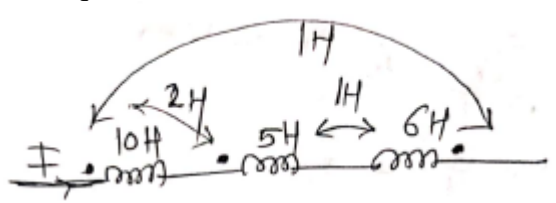
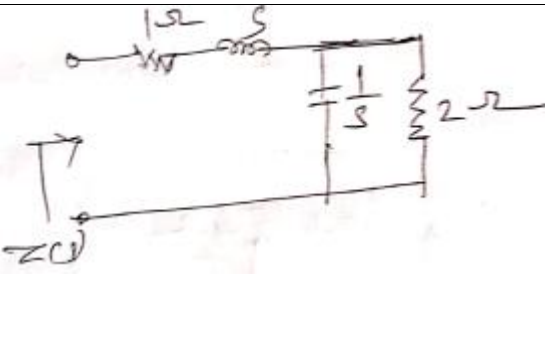
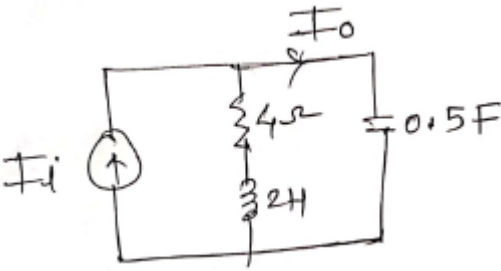





University of Mumbai
Examination 2020 under Cluster 06
(Lead College: Vidyavardhini's College of Engg Tech)
Examinations Commencing from 7th January 2021 to 20th January 2021
Program: Electronics Engineering
Curriculum Scheme: Rev 2019
Examination: SE Semester III

Course Code: ELC304 and Course Name: **Electrical Networks Analysis and Synthesis**
 Time: 2 hour Max. Marks: 80

Q1.	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks
1.	Which is the condition of symmetry for h parameters
Option A:	$h_{12} = -h_{21}$
Option B:	$h_{11}h_{22} - h_{12}h_{21} = 1$
Option C:	$h_{11}h_{21} - h_{12}h_{22} = 1$
Option D:	$h_{11} = 22$
2.	A dependent source
Option A:	May be a current source or a voltage source
Option B:	Is always a voltage source
Option C:	Is always a current source
Option D:	Neither a current source nor a voltage source
3.	<p style="text-align: center;">Find z parameters.</p>
Option A:	$\begin{bmatrix} 6 & 4 \\ 4 & 7 \end{bmatrix}$
Option B:	$\begin{bmatrix} 4 & 6 \\ 6 & 7 \end{bmatrix}$

Option C:	$\begin{bmatrix} 4 & 6 \\ 4 & 6 \end{bmatrix}$
Option D:	$\begin{bmatrix} 6 & 4 \\ 7 & 4 \end{bmatrix}$
4.	Application of Norton's theorem to a circuit yields
Option A:	Equivalent current source and impedance in series
Option B:	Equivalent current source and impedance in parallel
Option C:	Equivalent impedance
Option D:	Equivalent current source
5.	In time domain analysis, the initial condition from $t = -\infty$ to $t = 0^-$ denotes
Option A:	Just after switching condition
Option B:	Steady State Condition
Option C:	After switching condition
Option D:	Just before switching condition
6.	Which is this function $z(s) = \frac{4(s^2+1)(s^2+9)}{s(s^2+4)}$
Option A:	RC Function
Option B:	RL Function
Option C:	LC Function
Option D:	RLC Function
7.	Find equivalent inductance. 
Option A:	12 H
Option B:	13 H
Option C:	15 H
Option D:	21 H
8.	Find driving point impedance $Z(S)$.


	
Option A:	$\frac{2s^2 - 3s + 3}{2s + 1}$
Option B:	$\frac{2s^2 + 3s + 3}{2s + 1}$
Option C:	$\frac{2s^2 + 3s - 3}{2s + 1}$
Option D:	$\frac{2s^2 - 3s - 3}{2s + 1}$
9.	The necessary and sufficient condition for a rational function $F(S)$ to be the driving point impedance of an RC network is that all poles and zeros should be
Option A:	Simple and lie on the negative real axis in the s plane.
Option B:	Complex and lie in the left half of s plane.
Option C:	Complex and lie in the right half of s plane.
Option D:	Simple and lie on the positive real axis of the s plane.
10.	For the given network find poles and zeros of function I_o/I_i
	
Option A:	Zeros at $-0, -2$ and poles at $1, 1$
Option B:	Zeros at $0, -2$ and poles at $1, 1$
Option C:	Zeros at $0, -2$ and poles at $-1, -1$
Option D:	Zeros at $0, 2$ and poles at $-1, -1$
11.	Which is the condition of symmetry for ABCD parameters
Option A:	$AD - BC = 1$
Option B:	$B = C$
Option C:	$AB - CD = 1$
Option D:	$A = D$

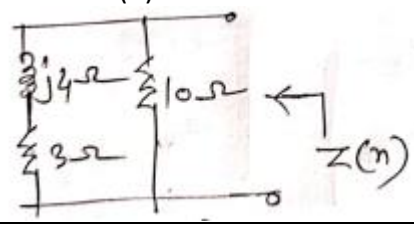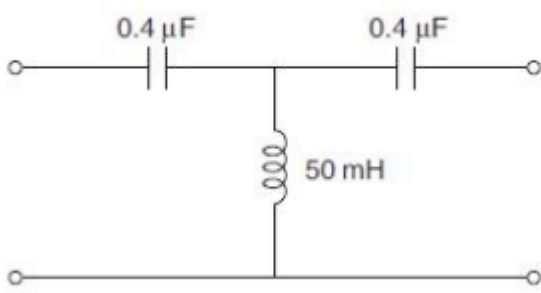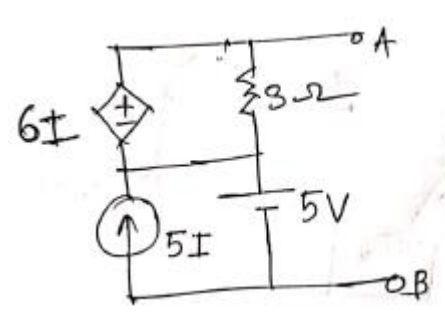12.	Calculate $Z(n)$ 
Option A:	3.86 angle 36.03^0 ohm
Option B:	3.86 angle -36.03^0 ohm
Option C:	3.68 angle 36.03^0 ohm
Option D:	3.68 angle -36.03^0 ohm
13.	The concept on which superposition theorem based is
Option A:	Reciprocity
Option B:	Duality
Option C:	Non-linearity
Option D:	Linearity
14.	The cut-off frequency of given circuit is 
Option A:	3.183 kHz
Option B:	795.77 Hz
Option C:	1.591 kHz
Option D:	253.3 Hz
15.	Find the voltage V_{AB} 
Option A:	11 I
Option B:	3+6 I
Option C:	6 I+5
Option D:	31 I
16.	Two identical sections of the network are connected in cascade having ABCD parameters as




	$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 7 & 8 \\ 2.5 & 3 \end{bmatrix}$ <p>Find Overall ABCD parameters</p>
Option A:	$\begin{bmatrix} 80 & 69 \\ 25 & 29 \end{bmatrix}$
Option B:	$\begin{bmatrix} 69 & 25 \\ 80 & 29 \end{bmatrix}$
Option C:	$\begin{bmatrix} 29 & 25 \\ 80 & 69 \end{bmatrix}$
Option D:	$\begin{bmatrix} 69 & 80 \\ 25 & 29 \end{bmatrix}$
17.	Kirchhoff's current law states that
Option A:	Net current flow at the junction is positive
Option B:	Algebraic sum of the currents meeting at the junction is zero
Option C:	No current can leave the junction without some current entering it
Option D:	Current can leave the junction without some current entering it
18.	At $t = 0^-$, No saturation condition has been reached. At $t = 0$, Switching action for application of DC source to inductive circuit. At $t = 0^+$, What will be the status of inductor?
Option A:	As it is
Option B:	Open Circuit
Option C:	Short Circuit
Option D:	Current Source
19.	In Maximum Power Transfer Theorem P_{max} is
Option A:	$\frac{V_{th}}{2R_{th}}$
Option B:	$\frac{V_{th}^2}{2R_{th}}$
Option C:	$\frac{V_{th}^2}{4R_{th}}$
Option D:	$\frac{V_{th}^2}{2RL}$

20.	<p>For the given ladder network which is not correct.</p>
Option A:	$V_C = V_2$
Option B:	$V_b = V_2$
Option C:	$V_a = V_b$
Option D:	$V_a = 2sI_a + V_b$

Q2 (20 Marks)	
A	Solve any Two 5 marks each
i.	<p>Test Whether the given function is positive real function.</p> $F(s) = \frac{2s^3 + 2s^2 + 3s + 2}{s^2 + 1}$
ii.	<p>Synthesis in Cauer II</p> $Z(s) = \frac{(s+1)(s+3)}{s(s+2)}$
iii.	<p>Synthesis in Cauer I</p> $Z(s) = \frac{(s^2+1)(s^2+9)}{s(s^2+4)}$
B	Solve any One 10 marks each
i.	<p>Determine Y and ABCD parameters</p>
ii.	Find Z- parameters

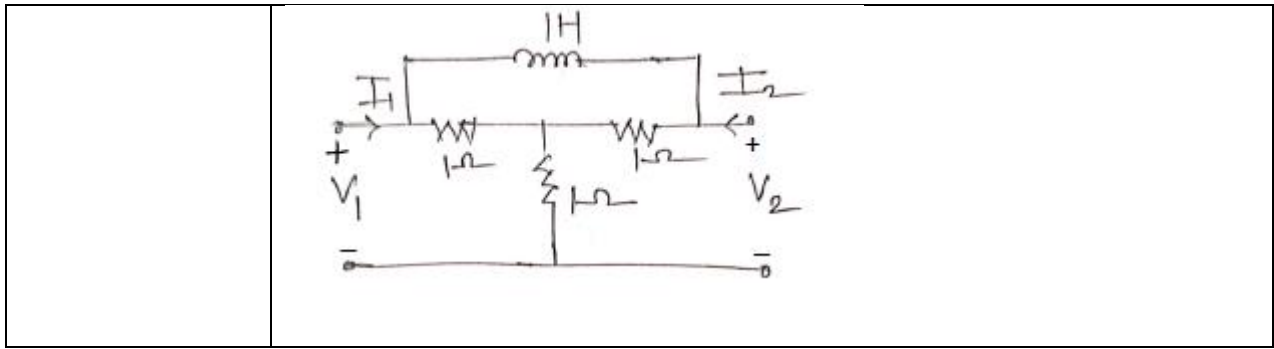

Q3 (20 Marks)	
A	Solve any Two 5 marks each
i.	<p>In the network shown in figure the switch is changed from the position 1 to the position 2 at $t = 0$, steady state condition having reached before switching. Find values of i, di/dt, and d^2i/dt^2. At $t = 0^+$</p>
ii.	<p>For the network shown in figure, find the response $V_0(t)$</p> <p>$V_s(t) = \frac{1}{2} \cos t u(t)$</p>

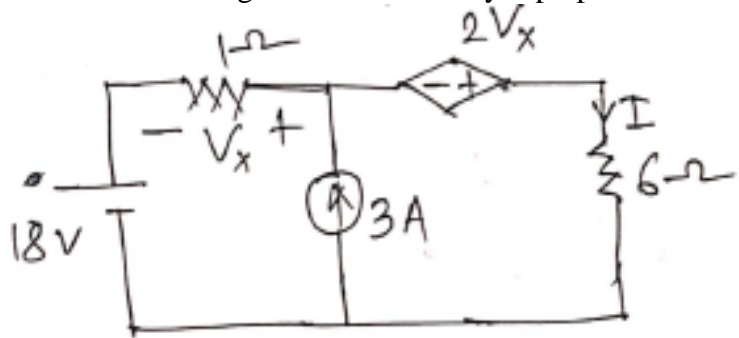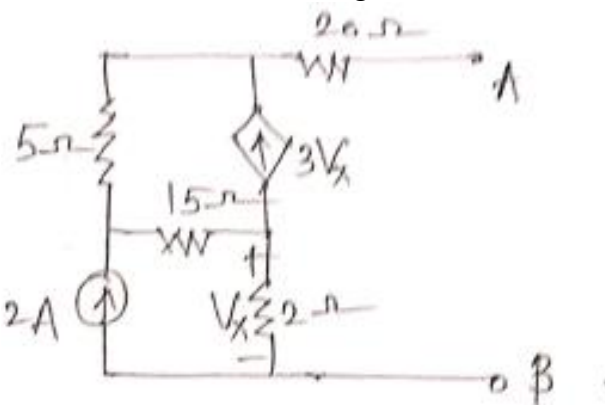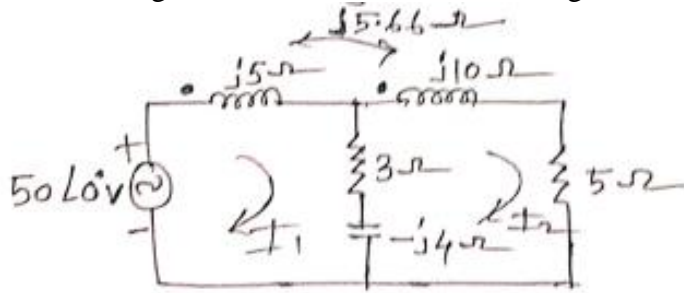iii.	<p>Find the current through 6 ohm resistor by superposition theorem.</p> 
B	<p>Solve any One 10 marks each</p>
i.	<p>For the network shown in figure. Find Norton's equivalent network.</p> 
ii.	<p>Find the voltage across the 5 ohm resistor using mesh analysis.</p> 

University of Mumbai
Examination 2020 under Cluster 06
(Lead College: Vidyavardhini's College of Engg Tech)
Examination Commencing from 7th January 2021 to 20th January 2021
Program: **Electronics Engineering**
Curriculum Scheme: Rev 2019
Examination: SE Semester III
Course Code: ELC303 and Course Name: Digital Logic Circuits

Time: 2 hour

Max. Marks: 80


Q1.	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks
1.	What is the decimal equivalent of $(11111)_2$.
Option A:	$(41)_{10}$
Option B:	$(21)_{10}$
Option C:	$(31)_{10}$
Option D:	$(11)_{10}$
2.	What is the reflected binary code of $(100101)_2$.
Option A:	111000
Option B:	101010
Option C:	101111
Option D:	110111
3.	Given the two binary numbers $x=1010100$ and $y=1000011$ perform the subtraction $x-y$, using 2's complement.
Option A:	0010001
Option B:	1101110
Option C:	1111111
Option D:	0000111
4.	How many two-input AND and OR gates are required to realize $Y = AB+CD+E$?
Option A:	2,2
Option B:	2,3
Option C:	3,2
Option D:	3,3
5.	If a half adder has A and B as the inputs, then the sum is given by
Option A:	A EX-NOR B
Option B:	A OR B
Option C:	A AND B
Option D:	A XOR B
6.	What are the number of select lines required for a 8:1 multiplexer?
Option A:	1
Option B:	2

Option C:	3
Option D:	4
7.	A decoder converts 'n' inputs to _____ number of outputs.
Option A:	2^n
Option B:	n
Option C:	n^2
Option D:	2n
8.	A basic latch circuit consists of
Option A:	one comparator
Option B:	three adders
Option C:	two inverters
Option D:	one amplifier
9.	A 'n-stage' Johnson counter will circulate a single data bit giving sequence of ____ number of states.
Option A:	2n
Option B:	n
Option C:	n+1
Option D:	n^2
10.	A decade counter can be implemented with how many number of flip flops?
Option A:	10
Option B:	5
Option C:	4
Option D:	8
11.	MSI counter IC74163 is
Option A:	4 bit up counter with synchronous preset and clear
Option B:	ripple counter
Option C:	decade counter
Option D:	4 bit up counter with asynchronous preset and clear
12.	In a sequential circuit designed as a moore machine, the output depends on
Option A:	present state
Option B:	past state
Option C:	next state
Option D:	external inputs
13.	IC 7490 is a
Option A:	Group A Asynchronous counter IC
Option B:	Group B Asynchronous counter IC
Option C:	Group C Asynchronous counter IC
Option D:	synchronous counter
14.	The internal structure of MSI counter IC 7493 consist of
Option A:	Mod 2 and Mod 6 counter
Option B:	Mod 2 and Mod 8 counter

Option C:	Mod 5 and Mod 8 counter
Option D:	Mod 2 and Mod 5 counter
15.	An AND gate with 8 input has a fan-out of
Option A:	8
Option B:	4
Option C:	2
Option D:	1
16.	What does FPGA stand for
Option A:	Field Programming Gate Array
Option B:	Field Programmable Gate Array
Option C:	First Program Gate Array
Option D:	First Programmable Gate Array
17.	Programmable Array Logic has
Option A:	a programmable AND and fixed OR array
Option B:	a programmable AND and a programmable OR array
Option C:	only a programmable AND array
Option D:	only a programmable OR array
18.	In verilog HDL the operator <= is used for
Option A:	Blocking assignment
Option B:	Non-Blocking assignment
Option C:	Single line comment
Option D:	Logical left shift
19.	Which type of modeling style is not used in verilog hardware description language
Option A:	Structural
Option B:	Datatype
Option C:	Behavioral
Option D:	Data Flow
20.	The Verilog expression for Boolean equation $Y=AB+C$ will be
Option A:	assign $Y= (A*B)+C$
Option B:	assign $Y= (A.B)+C$
Option C:	assign $Y= (A^B) C$
Option D:	assign $Y= (A\&B) C$

Q2. (20 Marks Each)	
A	Solve any Two 5 marks each
i.	Design and implement a half adder using gates.
ii.	State and prove De-Morgan's theorem.
iii.	Compare mealy and moore machines.
B	Solve any One 10 marks each
i.	Design a Mod-10 asynchronous counter using J-K Flip-Flops.
ii.	Write a program using Verilog HDL to implement a 8:1 multiplexer.

Q3. (20 Marks Each)	
A	Solve any Two 5 marks each
i.	Write a short note on Complex Programmable Logic Devices.
ii.	Convert a JK Flip-Flop to T Flip-Flop.
iii.	Write a program for a D flip-flop with asynchronous reset using Verilog HDL.
B	Solve any One 10 marks each
i.	Design and implement full subtractor circuit using a 3:8 decoder IC 74138.
ii.	Analyze the given state machine and draw the state diagram.

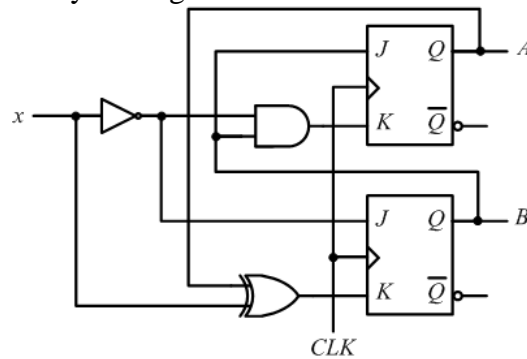

University of Mumbai
Examination 2020 under Cluster 06
(Lead College :- Vidyavardhini's College of Engineering & Technology)

Examinations Commencing from 7th January 2021 to 20th January 2021

Program: **Electronics Engineering**

Curriculum Scheme: Rev. 2019

Examination: S.E. Semester III

Course Code: ELC302 and Course Name: Electronic Devices & Circuits – I

Time: 2 hour

Max. Marks: 80

Q.1	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks.
1.	The capacitance in a reverse biased PN junction is called as :-
Option A:	Terminal capacitance
Option B:	Junction capacitance
Option C:	Diffusion capacitance
Option D:	Transition capacitance
2.	In any semiconductor material, the diffusion current is proportional to :-
Option A:	Applied electric field
Option B:	Concentration gradient of charge carriers
Option C:	Square of applied electric field
Option D:	Cube of applied electric field
3.	The phenomenon of Zener breakdown occurs in :-
Option A:	Heavily doped PN junction
Option B:	Lightly doped PN junction
Option C:	Moderately doped PN junction
Option D:	Forward biased PN junction
4.	Forward break-over voltage (V_{FBO}) of a typical silicon diode is approximately :-
Option A:	0.6 V – 0.7 V
Option B:	0.2 V – 0.3 V
Option C:	1.1 V – 1.2 V
Option D:	0.1 V – 0.2 V
5.	When a reverse current in Zener diode increases from 20 mA to 30 mA, Zener voltage changes from 5.6 V to 5.65 V. The Zener resistance (r_z) is given by :-
Option A:	2 Ω
Option B:	3 Ω
Option C:	4 Ω
Option D:	5 Ω
6.	In bipolar junction transistor (BJT) which mode of operation is not commonly used in real life applications ?
Option A:	The inverse / reverse mode of operation
Option B:	The cut-off mode of operation
Option C:	The saturation mode of operation
Option D:	The forward active / linear mode of operation

7.	In bipolar junction transistor (BJT) the Early effect is due to :-
Option A:	Decrease in width of the emitter due to reverse bias of collector-to-base junction
Option B:	Decrease in width of the base due to reverse bias of collector-to-base junction
Option C:	Decrease in width of collector due to reverse bias of collector-to-base junction
Option D:	Temperature variations resulting in thermally generated minority carriers
8.	In PNP bipolar junction transistor (BJT), stream of current in active region is due to :-
Option A:	Drift of holes
Option B:	Drift of electrons
Option C:	Diffusion of holes
Option D:	Diffusion of electrons
9.	In a bipolar junction transistor (BJT) if $\beta = 100$ & collector current (I_C) is 30 mA then what is the value of base current (I_B) ?
Option A:	0.03 mA
Option B:	0.3 mA
Option C:	3 mA
Option D:	300 mA
10.	The field effect transistor (FET) is :-
Option A:	Power controlled device
Option B:	Energy controlled device
Option C:	Current controlled device
Option D:	Voltage controlled device
11.	Pinch-off voltage in field effect transistor (FET) is :-
Option A:	Drain-to-source voltage giving zero (no) drain-to-source current
Option B:	Drain-to-source voltage giving maximum drain-to-source current
Option C:	Gate-to-source voltage giving zero (no) drain-to-source current
Option D:	Gate-to-source voltage giving maximum drain-to-source current
12.	Which of the following statement is not true for any field effect transistor (FET) ?
Option A:	FET has very high input resistance / impedance as compared to BJT
Option B:	FET is a majority carrier operated (unipolar) device
Option C:	FET has excellent operating stability against temperature variations compared to BJT
Option D:	FET has higher transconductance compared to BJT
13.	In junction field effect transistor (JFET), the amplification factor (μ) is expressed by which of the following mathematical expressions ?
Option A:	$\mu = g_m \times r_d$
Option B:	$\mu = g_m + r_d$
Option C:	$\mu = g_m - r_d$
Option D:	$\mu = g_m / r_d$
14.	For metal oxide semiconductor field effect transistor (MOSFET), the input impedance or the input resistance (R_i or Z_i) is :-
Option A:	Less than JFET but more than BJT
Option B:	More than both, JFET & BJT
Option C:	More than JFET but less than BJT
Option D:	Less than both, JFET & BJT
15.	In MOSFET, which terminal is electrically isolated from the entire device structure ?

Option A:	Source (S)
Option B:	Drain (D)
Option C:	Gate (G)
Option D:	Bulk or Body or Substrate (SS)
16.	In design of filters, which of these has the lowest value of ripple factor (γ) ?
Option A:	Capacitor (C) Filter
Option B:	Inductor (L) Filter
Option C:	Inductor & Capacitor (L-C) Filter
Option D:	C-L-C or ' π ' Filter
17.	Maximum operating efficiency of a full wave bridge type rectifier to be considered during the design process is :-
Option A:	25 %
Option B:	40.6 %
Option C:	81.2 %
Option D:	50 %
18.	Which of these statements is not true for any type of BJT common base (CB) configuration amplifier ?
Option A:	It has a low input impedance / resistance
Option B:	It has a high output impedance / resistance
Option C:	It has moderate to high voltage gain
Option D:	It produces a phase shift in amplified output signal with respect to input signal applied
19.	Which process of electron-hole pair (EHP) is responsible for emitting of light ?
Option A:	Recombination
Option B:	Diffusion
Option C:	Breakdown
Option D:	Ionization
20.	Which of these diodes does not work in the reverse bias mode of operation ?
Option A:	Light emitting diode (LED)
Option B:	Zener diode
Option C:	Varactor diode
Option D:	Photo diode

Q.2 (20 Marks)	Solve any Four out of Six	05 Marks Each
A	Explain the effects of temperature on the V – I characteristics of PN junction diode with a neat sketch / diagram & appropriate mathematical expressions.	
B	Describe forward bias V – I characteristics of PN junction diode with neat labeled diagram & appropriate sketch.	
C	Explain working of Center Tap type full wave rectifier with help of circuit diagram.	
D	Discuss the working / operation of dual end clipper circuit with a neat labeled diagram showing appropriate waveforms of the resulting clipped output voltage.	
E	Explain the operation of Zener diode as a voltage regulator with a neat sketch for condition where supply / source voltage remains constant but load resistor varies.	
F	With a neat sketch, describe the operating principle & the construction of the light emitting diode (LED).	

Q.3
(20
Marks)

Solve any Two out of Three

10 Marks Each

For a voltage divider bias circuit shown in Fig. 1 using Silicon (Si) BJT with $\beta = 100$ calculate the Q – point where $Q = [V_{CE}, I_C]$.

A

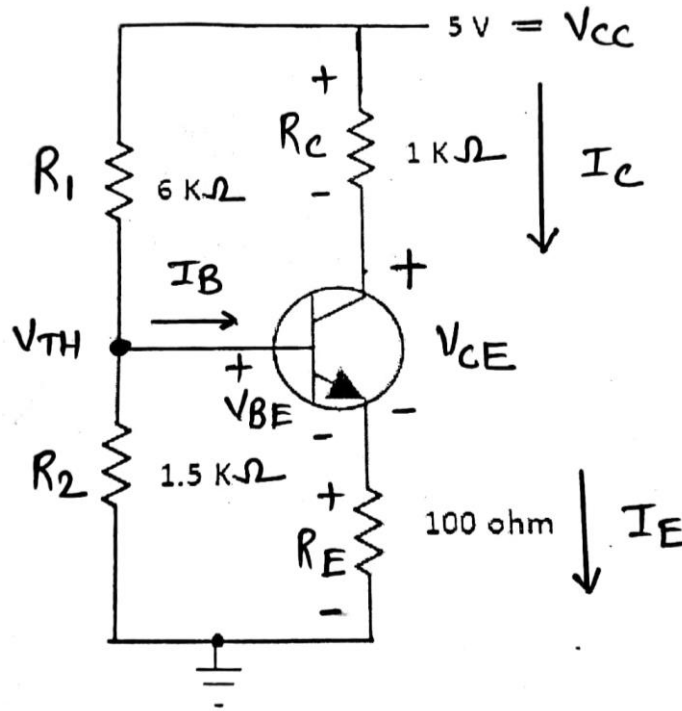


Fig. 1 for Q.3 (A)

For the voltage divider bias circuit shown in Fig. 2 using N-channel E-MOSFET calculate Q – point where $Q = [V_{DS}, I_D]$.

B

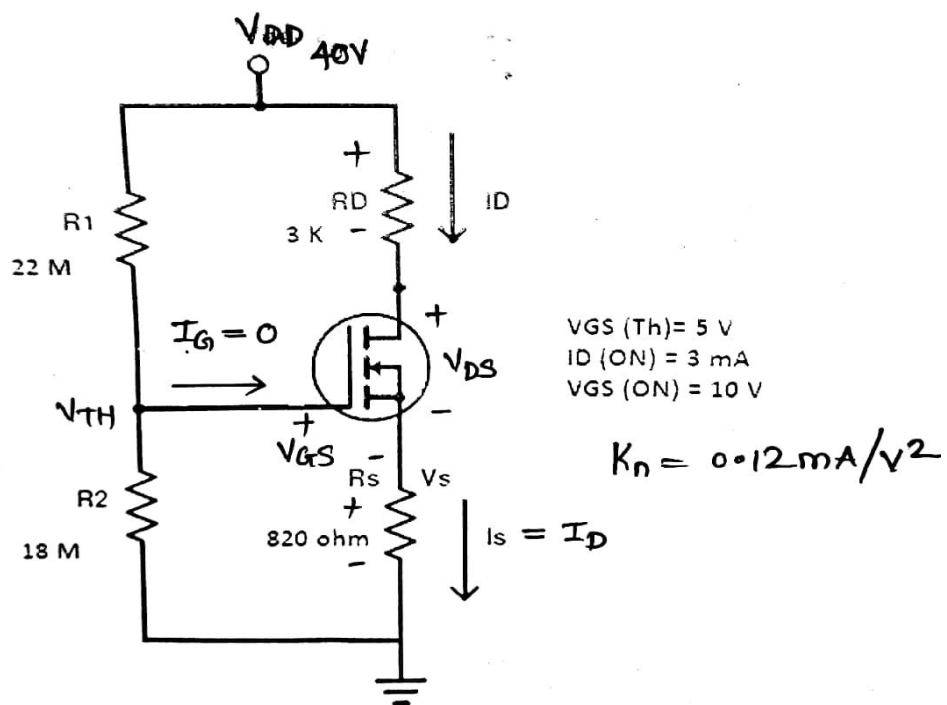


Fig. 2 for Q.3 (B)

Fig. 3 shows a single stage CE – BJT amplifier using BC 547 where $\beta = 300$ & $V_{BE} = 0.7$ V. Calculate the input resistance (R_i), output resistance (R_o) & small signal voltage gain (A_v).

C

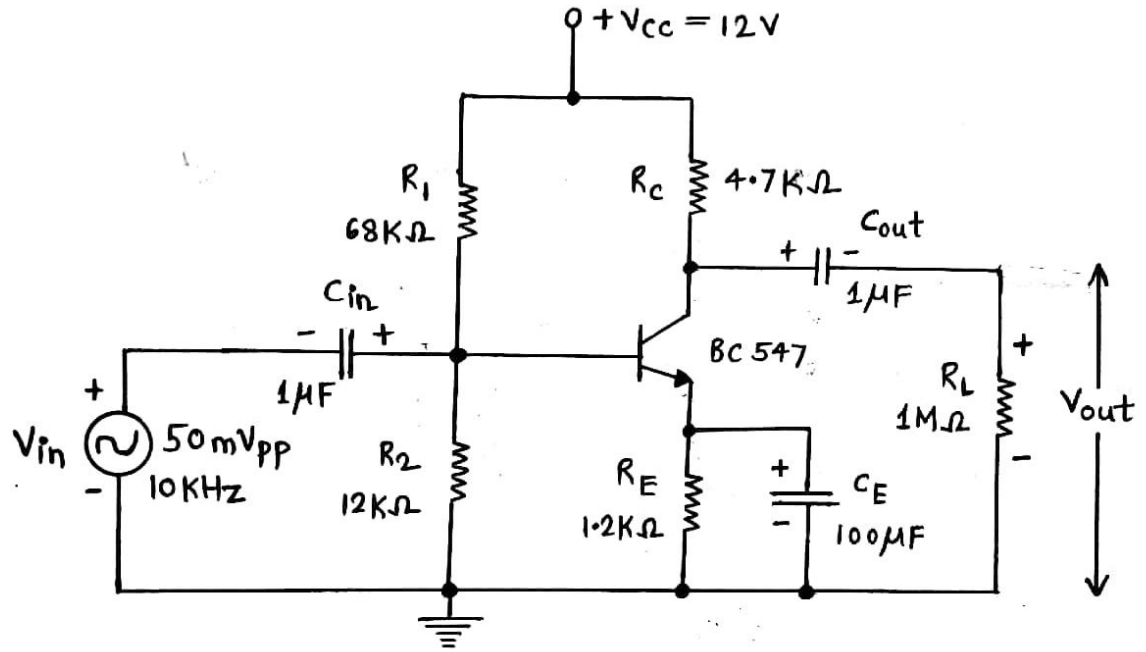


Fig. 3 for Q.3 (C)

University of Mumbai

Examinations Commencing from 7th January 2021 to 20th January 2021

Program: BE Electronics Engineering

Curriculum Scheme: Rev 2019 'C' Scheme

Examination: SE Semester III

Course Code: ELC301 and Course Name: Engineering Mathematics III

Time: 2 hour

Max. Marks: 80

Note : Q1 carrying 40 marks. Q2 and Q3 are carrying 20 equal marks.

Q1.	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks
1.	Find Laplace transform of $f(t) = 1, 0 < t < 5; f(t) = 0, t > 0$
Option A:	$\frac{1 - e^{-5s}}{s}$
Option B:	$\frac{1}{s} e^{-5s}$
Option C:	$\frac{1}{s}$
Option D:	$\frac{1 + e^{-5s}}{s}$
2.	If $L[f(t)] = \log\left(\frac{s+3}{s+1}\right)$, find $L[f(2t)]$
Option A:	$2 \log\left(\frac{s+3}{s+1}\right)$
Option B:	$2 \log\left(\frac{s+6}{s+2}\right)$
Option C:	$\frac{1}{2} \log\left(\frac{s+3}{s+1}\right)$
Option D:	$\frac{1}{2} \log\left(\frac{s+6}{s+1}\right)$
3.	Find $L[te^{-3t} \sin t]$
Option A:	$\frac{2s-6}{(s^2-6s+10)^2}$
Option B:	$\frac{2s+6}{(s^2+6s+10)^2}$
Option C:	$\frac{1}{(s+3)^2+1}$
Option D:	$\frac{1}{(s^2-6s+10)^2}$
4.	Find $L\left[\int_0^t u \sin 3u du\right]$
Option A:	$\frac{2}{(s^2+1)^2}$
Option B:	$\frac{2}{(s^2+3)^2}$
Option C:	$\frac{6}{(s^2+9)^2}$

Option D:	$\frac{2s}{(s^2+1)^2}$
5.	$L^{-1} \left[\frac{s+5}{s^2-25} \right] = ?$
Option A:	$\cos 5t + 5 \sin 5t$
Option B:	$\cosh 5t + 5 \sinh 5t$
Option C:	$\cosh 5t + \sinh 5t$
Option D:	$\cos ht + 5 \sin ht$
6.	Find $L^{-1} \left[\frac{s-2}{s^2-4s+13} \right]$
Option A:	$e^{2t} \frac{\sin 3t}{3}$
Option B:	$e^{-2t} \frac{\sin 3t}{3}$
Option C:	$e^{2t} \sin 3t$
Option D:	$e^{2t} \cos 3t$
7.	In Fourier series of $f(x) = x \cos x$ in $(-\pi, \pi)$. The value of a_n is
Option A:	0
Option B:	$\frac{-1}{2}$
Option C:	$\frac{(-1)^n}{n^2-1}$
Option D:	$\frac{1}{n^2-1}$
8.	$f(x) = \begin{cases} \cos x, & -\pi < x < 0 \\ -\cos x, & 0 < x < \pi \end{cases}$ is
Option A:	Both even and odd function
Option B:	neither even nor odd
Option C:	odd function
Option D:	Even function
9.	The Fourier series for $f(x)$ in $(0, 2\pi)$ is $f(x) = \frac{\pi}{2} - \frac{1}{\pi} \sum_{n=1}^{\infty} \frac{1}{n^2} \cos nx$. Find the value of $\frac{1}{2\pi} \int_0^{2\pi} [f(x)]^2 dx$
Option A:	$\frac{\pi^3}{4} + \frac{1}{\pi} \sum_{n=1}^{\infty} \frac{1}{n^4}$
Option B:	$\frac{\pi^2}{4} + \frac{1}{2\pi^2} \sum_{n=1}^{\infty} \frac{1}{n^4}$
Option C:	$\frac{\pi^3}{2} - \frac{1}{\pi} \sum_{n=1}^{\infty} \frac{1}{n^4}$
Option D:	0
10.	A function $f(t)$ is periodic with period 2π if

Option A:	$f(t + 2\pi) = 0$
Option B:	$f(t + 2\pi) = 2\pi$
Option C:	$f(t + 2\pi) = f(2\pi)$
Option D:	$f(t + 2\pi) = f(t)$
11.	Which of the following functions is NOT analytic
Option A:	Sinhz
Option B:	Cosz
Option C:	\bar{z}
Option D:	$z^2 + z$
12.	For $f(z) = u + iv$ analytic, which of the following statement is correct
Option A:	$f(z)$ may satisfy Cauchy-Riemann equation.
Option B:	$f(z)$ is constant function
Option C:	$f(z) = 0$
Option D:	u, v both are harmonic
13.	Find k such that $f(z) = \frac{1}{2} \log(x^2 + y^2) + itan^{-1} \frac{kx}{y}$ is analytic
Option A:	$K=1$
Option B:	$K=-1$
Option C:	$K=0$
Option D:	$K=2$
14.	Find the characteristic roots of matrix A , Where $A = \begin{bmatrix} 3 & -1 & 1 \\ -1 & 5 & -1 \\ 1 & -1 & 3 \end{bmatrix}$
Option A:	$\lambda = 1, 2, 3$
Option B:	$\lambda = 1, 1, -2$
Option C:	$\lambda = 2, 3, 6$
Option D:	$\lambda = -2, -3, -6$
15.	$\lambda = 5$ is one of the eigenvalues of $A = \begin{bmatrix} 1 & 2 & 2 \\ 2 & 1 & 2 \\ 2 & 2 & 1 \end{bmatrix}$. Find the eigenvector corresponding to eigenvalue $\lambda = 5$ is
Option A:	$[1 \ -1 \ 0]'$
Option B:	$[1 \ 1 \ 1]'$
Option C:	$[1 \ -1 \ -1]'$
Option D:	$[1 \ 0 \ -1]'$

16.	If $A = \begin{bmatrix} 1 & 2 & 8 \\ 0 & -1 & 3 \\ 0 & 0 & 2 \end{bmatrix}$ Find Eigen Values of $A^2 + 3A + 2A^{-1} + I$
Option A:	7,-3,12
Option B:	6,-4,11
Option C:	1,-1,2
Option D:	7,-3,15
17.	If the matrix A has eigen value 1,1,5 then algebraic multiplicity of A for $\lambda = 1$ is
Option A:	-1
Option B:	0
Option C:	1
Option D:	2
18.	The divergence and curl of $\vec{a} = 2i - 3j + k$ is
Option A:	$\text{div } \vec{a}=0$, $\text{curl } \vec{a}=5$
Option B:	$\text{div } \vec{a}=2$, $\text{curl } \vec{a}=0$
Option C:	$\text{div } \vec{a}=3$, $\text{curl } \vec{a}=3$
Option D:	$\text{div } \vec{a}=0$, $\text{curl } \vec{a}=0$
19.	Find the value of a if $\vec{F} = (x - 2z)i + (y - 5x)j + (az + 2x)k$ is solenoidal
Option A:	$a = 2$
Option B:	$a = -2$
Option C:	$a = -4$
Option D:	$a = 4$
20.	Evaluate $\int_C y dx + x dy$ along $y = x^2$ from A(0,0) to B(1,1)
Option A:	0
Option B:	2xy
Option C:	-1
Option D:	1

Q2. (20 Marks Each)	Solve any Four out of Six	5 marks each
A	Find $L \left[e^{-t} \int_0^t e^u \cosh u \, du \right]$	
B	$L^{-1} \left[\log \left(1 + \frac{4}{s^2} \right) \right] s$	
C	Obtain the Fourier series for e^{-x} in $(0, 2\pi)$	
D	Find the analytic function $f(z)$ whose imaginary part is $e^{-x}(y \sin y + x \cos y)$	
E	Show that $A = \begin{bmatrix} 2 & -1 & 1 \\ -1 & 2 & -1 \\ 1 & -1 & 2 \end{bmatrix}$ satisfies Cayley-Hamilton theorem. Hence find A^{-1}	

F	Evaluate by using Green's theorem $\int_C (x^2 - y)dx + (2y^2 + x)dy$, where C is the closed region bounded by $y = 4$ and $y = x^2$
---	---

Q3. (20 Marks Each)	Solve any Four out of Six	5 marks each
A	Evaluate $\int_0^{\infty} e^{-3t} \left(\frac{\sinh t \sin t}{t} \right) dt$	
B	Find $L^{-1} \left[\frac{s}{(s^2 + 4s + 13)^2} \right]$	
C	Obtain the half range Fourier sine series expansion for $f(x) = (x - x^2)$ in $(0,2)$	
D	Obtain the orthogonal trajectories for the family of curves $e^{-x} \cos y = C$.	
E	Check whether the matrix $A = \begin{bmatrix} 2 & 3 & 4 \\ 0 & 2 & -1 \\ 0 & 0 & 1 \end{bmatrix}$ is diagonalizable	
F	Show that $\vec{F} = (y^2 - z^2 + 3yz - 2x)i + (3xz + 2xy)j + (3xy - 2xz + 2z)k$ is both irrotational and solenoidal.	