

University of Mumbai
Examination 2021 under cluster __ (Lead College: _____)
Examinations Commencing from 15th June 2021 to 24th June 2021

Program: BE (Electronics)

Curriculum Scheme: Rev 2016 (CBCGS)

Examination: SE Semester III

Course Code: ELX301 and Course Name: Applied Mathematics III

Time: 2 hour

Max. Marks: 80

Q1.	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks
1.	Find Laplace Transform of $e^{3t}H(t - 2)$.
Option A:	$e^{2(s+3)} \cdot \frac{1}{s+3}$
Option B:	$e^{-2(s-3)} \cdot \frac{1}{s-3}$
Option C:	$e^{2(s-3)} \cdot \frac{1}{s-3}$
Option D:	$e^{-2(s+3)} \cdot \frac{1}{s+3}$
2.	The Laplace transform of $e^{-3t} \operatorname{erf} \sqrt{t}$ is
Option A:	$\frac{1}{(s-4)\sqrt{s-3}}$
Option B:	$\frac{1}{(s-3)\sqrt{s-4}}$
Option C:	$\frac{1}{(s+4)\sqrt{s+3}}$
Option D:	$\frac{1}{(s+3)\sqrt{s+4}}$
3.	The value of the integral $\int_0^\infty e^{-t} \sinh 2t \sin 3t dt$ is
Option A:	$\frac{1}{5}$
Option B:	$\frac{1}{15}$
Option C:	$\frac{1}{25}$
Option D:	$\frac{1}{35}$
4.	The inverse Laplace transform of $\tan^{-1}(s)$ is
Option A:	$\frac{-\sin t}{t}$
Option B:	$\frac{e^{-4t} \cosh t}{t}$
Option C:	$\frac{e^{-4t} \sin t}{t}$

Option D:	$\frac{\sin t}{t}$
5.	The inverse Laplace transform of $\left[\frac{e^{-\pi s}}{s^2-2s+2}\right]$ is
Option A:	$e^{-(t+\pi)} \sin(t - \pi)H(t - \pi)$
Option B:	$e^{(t+\pi)} \sin(t + \pi)H(t + \pi)$
Option C:	$e^{(t-\pi)} \sin(t - \pi)H(t - \pi)$
Option D:	$e^{(t-\pi)} \sin(t + \pi)H(t + \pi)$
6.	The inverse Laplace transform of $\frac{1}{s\sqrt{s+4}}$ is
Option A:	$\frac{1}{2} \operatorname{erf}_c(2\sqrt{t})$
Option B:	$\frac{1}{2} \operatorname{erf}(2\sqrt{2t})$
Option C:	$\frac{1}{2} \operatorname{erf}(4\sqrt{t})$
Option D:	$\frac{1}{2} \operatorname{erf}(2\sqrt{t})$
7.	If $f(x) = x^2, -\pi < x < \pi$, then the value of $\sum_{n=1}^{\infty} \frac{1}{n^2}$ is
Option A:	$\frac{\pi^2}{8}$
Option B:	$\frac{\pi^2}{6}$
Option C:	$\frac{\pi^2}{12}$
Option D:	$\frac{\pi^4}{6}$
8.	The Fourier series expansion of $f(x) = \begin{cases} -c, & -1 < x < 0 \\ c, & 0 < x < 1 \end{cases}$ is
Option A:	$\frac{c}{4\pi} \left[\sin \pi x + \frac{1}{3} \sin 3\pi x + \frac{1}{5} \sin 5\pi x + \dots \right]$
Option B:	$\frac{4c}{\pi} \left[\cos \pi x + \frac{1}{3} \cos 3\pi x + \frac{1}{5} \cos 5\pi x + \dots \right]$
Option C:	$\frac{4c}{\pi} \left[\sin \pi x - \frac{1}{3} \sin 3\pi x + \frac{1}{5} \sin 5\pi x - \dots \right]$
Option D:	$\frac{4c}{\pi} \left[\sin \pi x + \frac{1}{3} \sin 3\pi x + \frac{1}{5} \sin 5\pi x + \dots \right]$
9.	The complex form of Fourier series for $f(x)=2x$ in $[0, 2\pi]$ is
Option A:	$2\pi + 2i \sum_{n=-\infty}^{\infty} \frac{e^{nix}}{n}, \quad \text{for } n \neq 0$
Option B:	$2\pi + 2i \sum_{n=-\infty}^{\infty} \frac{e^{-nix}}{n}, \quad \text{for } n \neq 0$

Option C:	$2\pi + 2i \sum_{n=-\infty}^{\infty} \frac{e^{nix}}{4n}, \quad \text{for } n \neq 0$
Option D:	$2\pi + 2i \sum_{n=-\infty}^{\infty} \frac{e^{-nix}}{8n}, \quad \text{for } n \neq 0$
10.	The half range sine series of $f(x)=x(\pi - x)$ in $(0, \pi)$ is
Option A:	$\frac{8}{\pi} \left[\frac{1}{1^4} \sin \pi x - \frac{1}{3^4} \sin 3\pi x + \frac{1}{5^4} \sin 5\pi x - \dots \right]$
Option B:	$\frac{8}{\pi} \left[\frac{1}{1^3} \sin \pi x + \frac{1}{3^3} \cos 3\pi x + \frac{1}{5^3} \sin 5\pi x + \dots \right]$
Option C:	$\frac{8}{\pi} \left[\frac{1}{1^3} \sin \pi x + \frac{1}{3^3} \sin 3\pi x + \frac{1}{5^3} \sin 5\pi x + \dots \right]$
Option D:	$\frac{8}{\pi} \left[\frac{1}{1^3} \cos \pi x + \frac{1}{3^3} \cos 3\pi x + \frac{1}{5^3} \cos 5\pi x + \dots \right]$
11.	The value of $[\bar{b} \times \bar{c} \quad \bar{a} \times \bar{c} \quad \bar{a} \times \bar{b}]$ is
Option A:	$-\left[\bar{a} \quad \bar{b} \quad \bar{c}\right]^2$
Option B:	$\left[\bar{a} \quad \bar{b} \quad \bar{c}\right]^2$
Option C:	$\left[\bar{a} \quad \bar{b} \quad \bar{c}\right]^3$
Option D:	$\left[\bar{a} \quad \bar{b} \quad \bar{c}\right]^4$
12.	The unit normal vector to the surface $xy^3z^2 = 4$, at $(-1, -1, 2)$ is
Option A:	$\frac{-(i + 3j - k)}{\sqrt{11}}$
Option B:	$\frac{(i + 3j - k)}{\sqrt{11}}$
Option C:	$\frac{-(i + 3j + k)}{\sqrt{11}}$
Option D:	$\frac{-(i - 3j - k)}{\sqrt{11}}$
13.	If $\bar{F} = (axy + bz^3)i + (3x^2 - cz)j + (3xz^2 - y)k$ is irrotational, then the value of a, b, c is
Option A:	$a = 6, b = 1, c = 6$
Option B:	$a = 1, b = 6, c = 1$
Option C:	$a = 1, b = 1, c = 6$
Option D:	$a = 6, b = 1, c = 1$
14.	Using Green's theorem, the value of $\int_C (P dx + Q dy)$ is
Option A:	$\iint_R \left(\frac{\partial Q}{\partial x} + \frac{\partial P}{\partial y} \right) dx dy$
Option B:	$\iint_R \left(\frac{\partial P}{\partial x} - \frac{\partial Q}{\partial y} \right) dx dy$

Option C:	$\iint_R \left(\frac{\partial Q}{\partial x} - \frac{\partial P}{\partial y} \right) dx dy$
Option D:	$-\iint_R \left(\frac{\partial Q}{\partial x} + \frac{\partial P}{\partial y} \right) dx dy$
15.	For any closed surface S, the value of $\iint_S (\nabla\phi \times \nabla\psi) \cdot d\bar{S}$ is
Option A:	0
Option B:	1
Option C:	-1
Option D:	∞
16.	Using Stokes's theorem, the value of $\int_c (x^2i + xyj) \cdot d\bar{r}$ where c is boundary of the rectangle $x = 0, y = 0, x = 2, y = 3$
Option A:	3
Option B:	6
Option C:	9
Option D:	18
17.	If the imaginary part of analytic function is $\tan^{-1} \left(\frac{y}{x} \right)$, then the analytic function must be
Option A:	$-\log z + c$
Option B:	$\log \sqrt{z} + c$
Option C:	$\tan(\log z) + c$
Option D:	$\log z + c$
18.	Which one of the following functions is Harmonic Function?
Option A:	$u = y^3 + 3x^2y$
Option B:	$u = y^3 - 3x^2y$
Option C:	$u = y^3 - x^2y$
Option D:	$u = y^3 - 3x^2$
19.	Find the fixed points of the bilinear transformation of $w = \frac{2z+6}{z+7}$
Option A:	1, -6
Option B:	-1, 6
Option C:	-1, -2
Option D:	1, -2
20.	The value of $J_n(x)$ is
Option A:	$\sum_{m=0}^{\infty} \frac{(-1)^m (x/2)^{2m+n}}{m! n+m-1 }$
Option B:	$\sum_{m=0}^{\infty} \frac{(-1)^m (x/2)^{2m-n}}{m! n+m+1 }$

Option C:	$\sum_{m=0}^{\infty} \frac{(-1)^m (x/2)^{2m+n}}{m! n+m+1 }$
Option D:	$\sum_{m=0}^{\infty} \frac{(-1)^m (x/2)^{2m+n}}{m! n-m+1 }$

Q2	Solve any Four out of Six	5 marks each
A	Find the Laplace transform of: $\cosh t \int_0^t e^u \cosh u \, du$	
B	Using convolution theorem, find inverse Laplace transforms of $\frac{1}{(s-2)(s+2)^2}$	
C	Find complex form of Fourier Series for $f(x)=e^{-x}$ in the interval $(-1,1)$	
D	Find $f(\mathbf{r})$, so that the vector $f(\mathbf{r})\bar{\mathbf{r}}$ is both solenoidal and irrotational	
E	Using stoke's theorem evaluate $\int_C \bar{\mathbf{F}} \cdot d\bar{\mathbf{r}}$ where $\bar{\mathbf{F}} = y\mathbf{i} + z\mathbf{j} + x\mathbf{k}$ and C is the boundary of the surface $x^2 + y^2 = 1 - z, \quad z > 0$	
F	Find the Bilinear Transformation which maps the points $z = \infty, i, 0$ onto the points $w = 0, i, \infty$.	

Q3	Solve any Four out of Six	5 marks each
A	Prove that $\int_0^{\infty} e^{-\sqrt{2}t} \left\{ \frac{\sin t \sinh t}{t} \right\} dt = \frac{\pi}{8}$	
B	Find inverse Laplace transform of $\frac{1}{(s+3)(s^2+2s+2)}$	
C	Find the Fourier series expansion of $f(x) = \begin{cases} 2, & -2 < x < 0 \\ x, & 0 < x < 2 \end{cases}$	
D	Find the angle between the surfaces $x \log z + 1 - y^2 = 0, \quad x^2 y + z = 2$ at $(1, 1, 1)$	
E	Using Gauss Divergence theorem, prove that $\iint (y^2 z^2 \mathbf{i} + z^2 x^2 \mathbf{j} + y^2 z^2 \mathbf{k}) \cdot \bar{\mathbf{N}} \, dS = \frac{\pi}{12}$ where S is the part of the sphere $x^2 + y^2 + z^2 = 1$ above the XY plane	
F	Prove that $J_{5/2}(x) = \sqrt{\frac{2}{\pi x}} \cdot \left\{ \frac{3-x^2}{x^2} \sin x - \frac{3}{x} \cos x \right\}$	

University of Mumbai
Examination 2021 under Cluster 06
(Lead College: Vidyavardhini's College of Engg Tech)

Examinations Commencing from 15th June 2021

Program: **Electronics Engineering**


Curriculum Scheme: Rev 2016

Examination: SE Semester III

Course Code: ELX302 and Course Name: Electronic Devices and Circuits-I

Time: 2 hour



Max. Marks: 80

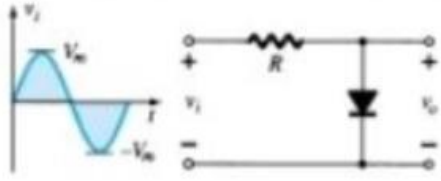
Q1. 40 Marks	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks
1.	Name the current produced due to motion of charge carriers from a region of higher concentration to a region of lower concentration?
Option A:	drift current
Option B:	diffusion current
Option C:	electron current
Option D:	hole current
2.	Why is the silicon mostly chosen when compared to germanium?
Option A:	low power consumption
Option B:	high efficiency
Option C:	greater working temperature
Option D:	large I_{CBO}
3.	If the temperature of a crystal diode increases, then leakage current-----
Option A:	remains the same
Option B:	decreases
Option C:	increases
Option D:	becomes zero
4.	Assume the diode is ideal. What will be the peak value of the output waveform for the given circuit. 
Option A:	V_m
Option B:	$-V_m$
Option C:	$+(V_m - V_d)$
Option D:	$-(V_m - V_d)$
5.	If the input junction and the output junction is forward biased, then the transistor is said to be in _____ region
Option A:	Active Region
Option B:	Cut off Region

Option C:	Breakdown Region
Option D:	Saturation Region
6.	For a Voltage divider circuit having $R_C=R_1=R_2=R_E=1K\Omega$, if $V_{CC}=20V$, find I_C when $V_{ce} = V_{cc}$.
Option A:	0
Option B:	2mA
Option C:	20mA
Option D:	1mA
7.	Input impedance Z_{in} for a voltage divider CE Amplifier is given as-----
Option A:	$Z_{in}=R_1\parallel R_2\parallel r_e$
Option B:	$Z_{in}=R_1\parallel R_2$
Option C:	$Z_{in}=R_1\parallel R_2\parallel r_{\pi}$
Option D:	$Z_{in}=R_1\parallel r_{\pi}$
8.	For a Voltage divider bias circuit, having $R_1=R_2=10K\Omega$, $R_C = 4.7 k\Omega$, $R_E=1 K\Omega$, What is the value of collector current at saturation if $V_{CC}=10V$?
Option A:	1A
Option B:	10mA
Option C:	1.75mA
Option D:	1mA
9.	Name this cumulative process of rise in temperature in BJT.
	<p>The diagram shows a cumulative process of rise in temperature in a BJT. It starts with three circles labeled 'T ↑' (Temperature increase) on the left. An arrow labeled 'Leads to' points to a circle labeled 'I_{cbo} ↑' (Collector-base leakage current increase). This leads to another 'I_{cbo} ↑' circle, which then leads to 'I_{ceo} ↑' (Collector-emitter current increase) circles. These lead to 'I_c ↑' (Collector current increase) circles, which finally lead back to 'T ↑' circles, completing the feedback loop.</p>
Option A:	Stabilization
Option B:	Thermal Runaway
Option C:	Early effect
Option D:	Base width modulation
10.	The capacitive reactance, X_C , of the bypass capacitor should be at least _____ times smaller than R_E at the minimum frequency for which the amplifier must operate.
Option A:	10
Option B:	100
Option C:	50
Option D:	500
11.	MOSFET is a _____ device
Option A:	Voltage Controlled
Option B:	Current Controlled
Option C:	Impedance Controlled

Option D:	Admittance Controlled
12.	What will be the current flowing through the gate terminal of an FET?
Option A:	IDSS
Option B:	IDSS/2
Option C:	IDSS/4
Option D:	zero
13.	The _____ can be operated in two modes: Depletion mode and enhancement mode.
Option A:	BJT
Option B:	JFET
Option C:	D-MOSFET
Option D:	Diode
14.	For levels of $V_{GS} > V_T$, the drain current is related to the applied gate-to-source voltage by the following nonlinear relationship: _____
Option A:	$I_D = k (V_{GS} - V_T)^2$
Option B:	$I_D = k (V_{GS} - V_T)$
Option C:	$I_D = (V_{GS} - V_T)^2$
Option D:	$I_D = k (V_{GS} - V_T^2)$
15.	If a MOSFET is to be used as an amplifier then it must work in _____
Option A:	Cut-off region
Option B:	Triode region
Option C:	Saturation region
Option D:	Both cut-off and triode region can be used
16.	_____ is a semiconductor formed by a junction of semiconductor with a metal.
Option A:	Schottky Diode
Option B:	Photo diode
Option C:	Tunnel diode
Option D:	Gunn diode
17.	Name the component placed in a counter system that helps in counting the objects as they are passing on a conveyor
Option A:	Solar Cell
Option B:	Schottky diode
Option C:	Photo diode
Option D:	LED
18.	Efficiency of center tapped full wave rectifier is _____
Option A:	81.2%
Option B:	50%
Option C:	40.6%
Option D:	45.3%
19.	What is the peak inverse voltage across diode for a center tapped full wave

	rectifier?
Option A:	V_m
Option B:	$2V_m$
Option C:	$V_m/2$
Option D:	$V_m/1.44$
20.	The value of inductance in LC filter at which the load current does not fall to zero is called -----
Option A:	Peak inductance
Option B:	Critical inductance
Option C:	Cut in inductance
Option D:	Damping inductance

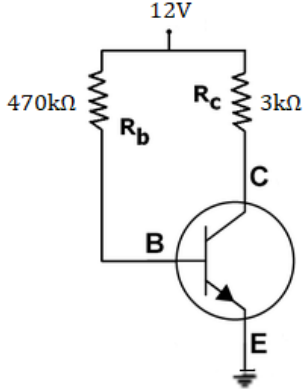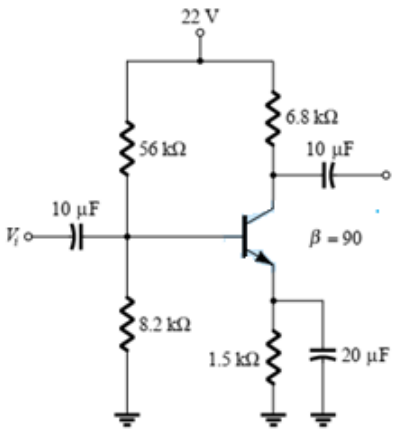Q2 (20 Marks)	
A	Solve any Two 5 marks each
i.	Explain the construction and working of JFET with neat diagrams.
ii.	Explain the operation of BJT as an amplifier.
iii.	Find I_{BQ} , I_{CQ} and V_{CEQ} for the given bias circuit. Given $\beta=100$
	
B	Solve any One 10 marks each
i.	Find Z_i , Z_o , A_v and A_i for the following circuit
	
ii.	Determine I_{DQ} , V_{GSQ} , and V_{DS} for the network given

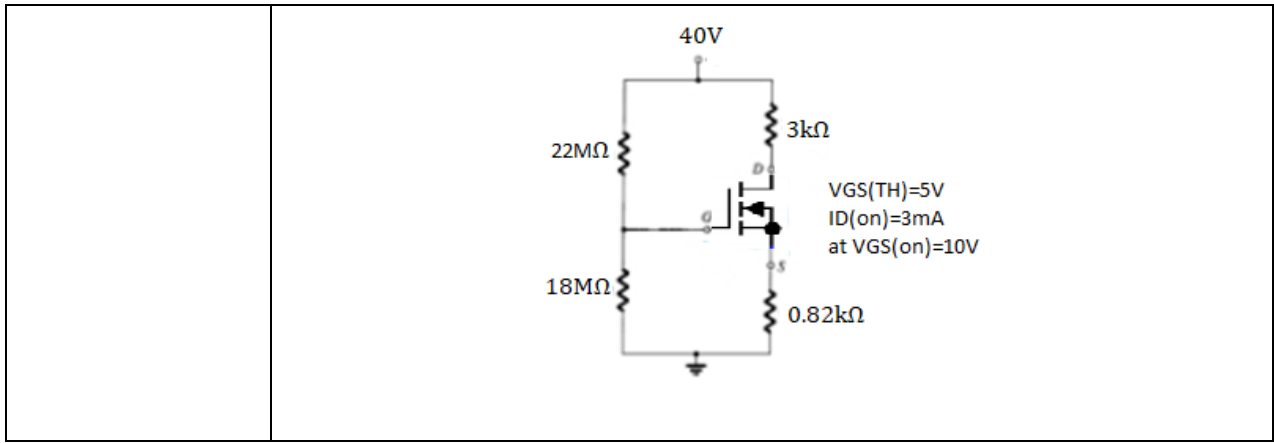

Q3 (20 Marks)	
A	Solve any Two 5 marks each
i.	Explain the VI characteristics of PN junction diode.
ii.	Compare HWR, Centre tapped FWR and Bridge Rectifier
iii.	Explain the construction, working and characteristics of Photodiode.
B	Solve any One 10 marks each
i.	Design a single stage CE Amplifier to give a voltage gain $A_v \geq 80$ with stability factor $S \leq 11$ and output voltage of, $V_o \text{ rms} = 3\text{V}$. Assume $V_{cc} = 18\text{V}$ and $V_{BE} = 0.7\text{V}$. Use npn transistor with specifications: $h_{fe} (\text{min}) = 115$, $h_{fe} (\text{typ}) = 180$, $h_{ie} = 4.5\text{k}\Omega$, and frequency $f_L \leq 300\text{Hz}$.
ii.	Perform ac analysis on a bypassed CS D-MOSFET amplifier with voltage divider bias circuit with neat diagrams to obtain the expression for input impedance (Z_i), output impedance (Z_o) input and voltage gain (A_v).

University of Mumbai
Examination 2021 under Cluster 06
(Lead College: Vidyavardhini's College of Engg Tech)

Examination Commencing from 15th June 2021

Program: **Electronics Engineering**

Curriculum Scheme: Rev 2016

Examination: SE Semester III

Course Code: ELX303 and Course Name: Digital Circuit Design

Time: 2 hour

Max. Marks: 80

Q1.	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks
1.	Decimal number of binary number 10111 is
Option A:	21
Option B:	22
Option C:	23
Option D:	24
2.	Binary codes of octal no. (645) ₈ is
Option A:	110 100 110
Option B:	110 101 100
Option C:	110 101 100
Option D:	110 100 101
3.	(D8A) ₁₆ - (426) ₁₆ is
Option A:	965
Option B:	964
Option C:	963
Option D:	962
4.	Binary representation of gray no. 10110 is
Option A:	11011
Option B:	11001
Option C:	11010
Option D:	10110
5.	In BCD invalid codes are
Option A:	8 to 15
Option B:	7 to 14
Option C:	10 to 15
Option D:	11 to 15
6.	In Boolean algebra what is value of $A+AB=?$
Option A:	A+B
Option B:	A-B
Option C:	B
Option D:	A

7.	Which of the following expressions is in the sum-of-products form?
Option A:	$(A + B)(C + D)$
Option B:	$(A \cdot B)(C \cdot D)$
Option C:	$A \cdot B \cdot (CD)$
Option D:	$AB + CD$
8.	Don't care conditions can be used for simplifying Boolean expressions in _____
Option A:	Registers
Option B:	Terms
Option C:	K-maps
Option D:	Latches
9.	What is a multiplexer?
Option A:	It is a type of decoder which decodes several inputs and gives one output
Option B:	A multiplexer is a device which converts many signals into one
Option C:	It takes one input and results into many output
Option D:	It is a type of encoder which
10.	In a multiplexer, the selection of a particular input line is controlled by _____
Option A:	Data controller
Option B:	Selected lines
Option C:	Logic gates
Option D:	Both data controller and selected lines
11.	Which flip-flop is called as Delay Flip-Flop
Option A:	S—R FLIP FLOP
Option B:	J-KFLIP FLOP
Option C:	D FLIP FLOP
Option D:	T FLIP FLOP
12.	The word de-multiplexer means _____
Option A:	one in to many
Option B:	Many into one
Option C:	Distributor
Option D:	converter
13.	The full form of SR is _____
Option A:	System rated
Option B:	Set reset
Option C:	Set ready
Option D:	Set Rated
14.	The characteristic equation of S-R latch is _____
Option A:	$Q(n+1) = S + Q(n)R'$
Option B:	$Q(n+1) = SR + Q(n)R$
Option C:	$Q(n+1) = S'R + Q(n)R$

Option D:	$Q(n+1) = S'R + Q'(n)R$
15.	How is a J-K flip-flop made to toggle?
Option A:	J = 0, K = 0
Option B:	J = 1, K = 0
Option C:	J = 0, K = 1
Option D:	J = 1, K = 1
16.	BCD counter is also known as _____
Option A:	Parallel counter
Option B:	Decade counter
Option C:	Synchronous counter
Option D:	VLSI counter
17.	CMOS gates are commercially available as which of the following series?
Option A:	1000
Option B:	2000
Option C:	3000
Option D:	4000
18.	Which of the following is the most widely employed logic family?
Option A:	Emitter-coupled logic
Option B:	Transistor-transistor logic
Option C:	CMOS logic family
Option D:	NMOS logic
19.	The full form of SIPO is _____
Option A:	Serial-in Parallel-out
Option B:	Parallel-in Serial-out
Option C:	Serial-in Serial-out
Option D:	Serial-In Peripheral-Out
20.	What is the difference between a shift-right register and a shift-left register?
Option A:	There is no difference
Option B:	The direction of the shift
Option C:	Propagation delay
Option D:	The clock input

Q2 (20 Marks)	
A	Solve any Two 5 marks each
i.	Convert D flip flop to T flip flop.
ii.	Design FULL ADDER 3 lines to 8 lines decoder .
iii.	What is the difference between asynchronous counter and synchronous counter
B	Solve any One 10 marks each
i.	Design 2 bit synchronous counter using J-K flip-flop
ii.	Implement the expression using K-Map for the function $F(A,B,C,D) =$

	$\sum m(2,3,6,7,8,9,13,14)$
--	-----------------------------

Q3. (20 Marks)	
A	Solve any Two 5 marks each
i.	Draw and explain the circuit diagram of 2-input TTL NAND gate.
ii.	State and explain with examples DeMorgan's Law
iii.	Design 2 bit Grey Code Counter using T Flip-Flop
B	Solve any One 10 marks each
i.	Simplify 4 variable Boolean function using Quine-McClusky technique $F(A,B,C,D) = \sum m(0,1,2,3,8,9,10,11,12,13)$
ii.	Explain Lock-Out condition in counters with examples.

University of Mumbai
Examination 2021 under Cluster 06
(Lead College: Vidyavardhini's College of Engg Tech)

Examinations Commencing from 15th June 2021

Program: **Electronics Engineering**

Curriculum Scheme: **Rev 2016**



Examination: **SE Semester III**


Course Code: **ELX304** and Course Name: **Electrical Network Analysis and Synthesis**


Time: 2-hour

Max. Marks: 80

Q1.	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks
1.	In Superposition theorem, while considering a source, all other voltage sources are?
Option A:	open circuited
Option B:	short circuited
Option C:	change its position
Option D:	removed from the circuit
2.	The maximum possible mutual inductance of two inductively coupled coils with self-inductances $L_1 = 25 \text{ mH}$ & $L_2 = 100 \text{ mH}$ is given by
Option A:	125 mH
Option B:	75 mH
Option C:	50 mH
Option D:	20 mH
3.	For transfer of maximum power, the relation between load resistance R and internal resistance r of the voltage source is
Option A:	$R = 2r$
Option B:	$R = 1.5r$
Option C:	$R = r$
Option D:	$R = 0.5r$
4.	In the circuit shown, find the current through 3Ω resistor using Superposition theorem.
Option A:	6
Option B:	5
Option C:	5.6
Option D:	6.5

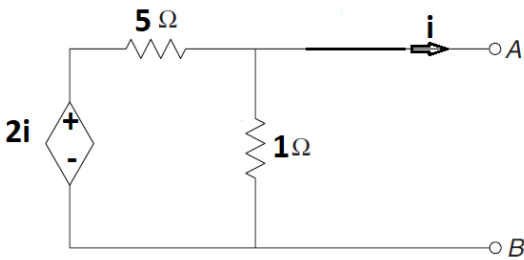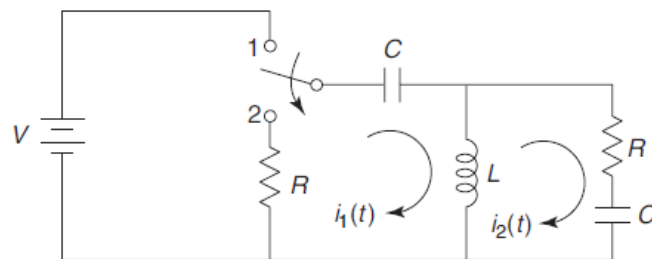5.	For transfer of maximum power, the relation between load resistance R and internal resistance r of the voltage source is
Option A:	$R = 2r$
Option B:	$R = 1.5r$
Option C:	$R = r$
Option D:	$R = 0.5r$
6.	Norton's current in the following figure is _____ 
Option A:	$2i/5$ Amp
Option B:	Zero
Option C:	Infinite
Option D:	$2i/6$ Amp
7.	Superposition theorem states that the response in any element is the _____ of the responses that can be expected to flow if each source acts independently of other sources.
Option A:	Algebraic sum
Option B:	Vector sum
Option C:	Multiplication
Option D:	Subtraction
8.	At $t = 0^-$ No saturation condition has been reached. At $t = 0$ Switching action for application of DC source to capacitive circuit. At $t = 0^+$ What will be the status of inductor?
Option A:	As it is
Option B:	Open Circuit
Option C:	Short Circuit
Option D:	Current Source
9.	At $t = 0^+$ the current i_1 in figure is 
Option A:	$-V / 2R$
Option B:	$-V / R$
Option C:	$-V / 4R$

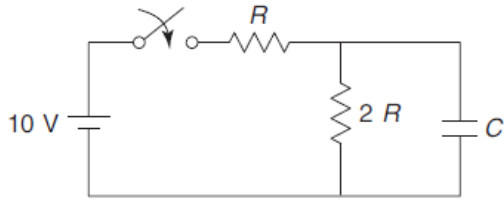Option D:	Zero
10.	The time constant of the network shown in figure is 
Option A:	2RC
Option B:	3RC
Option C:	RC (1 / 2)
Option D:	RC (2 / 3)
11.	In series RC circuit the time constant 'T' is given by –
Option A:	CR
Option B:	R / C
Option C:	C / R
Option D:	R+ C
12.	If excitation and response are measured at the same ports, the network function is known as
Option A:	RL network only
Option B:	RC network only
Option C:	LC network only
Option D:	RL as well as RC network
13.	The condition for reciprocity of Y parameters –
Option A:	$Y_{12} = Y_{21}$
Option B:	$Y_{11} = Y_{22}$
Option C:	$Y_{12} \cdot Y_{21} = 1$
Option D:	$Y_{11} \cdot Y_{22} = 1$
14.	The condition for symmetry of Z parameters –
Option A:	$Z_{12} = Z_{21}$
Option B:	$Z_{11} = Z_{22}$
Option C:	$Z_{12} \cdot Z_{21} = 1$
Option D:	$Z_{11} \cdot Z_{22} = 1$
15.	The necessary and sufficient condition for a rational function F(s) to be the driving-point impedance of an RC network is that all poles and zeros should be
Option A:	simple and lie on the negative real axis in the s-plane
Option B:	complex and lie in the left half of s-plane
Option C:	complex and lie in the right-half of s-plane
Option D:	simple and lie on the positive real axis of the s-plane
16.	The number of roots of $S^3 + 5S^2 + 7S + 3 = 0$ in the left half of s-plane is
Option A:	Zero
Option B:	One
Option C:	Two

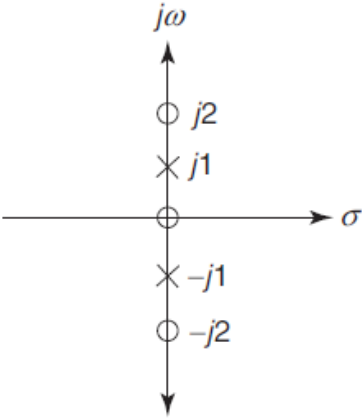Option D:	Three
17.	The pole-zero pattern of a particular network is shown in Figure. It is that of an 
Option A:	LC Network
Option B:	RC Network
Option C:	RL Network
Option D:	Only Resistive Network
18.	Filter have the -
Option A:	Characteristic impedance is resistive in stop band
Option B:	Characteristic impedance is reactive in pass band
Option C:	Characteristic impedance is resistive in pass band
Option D:	Characteristic impedance is infinite in stop band
19.	If f_1 and f_2 are the lower and upper cut off frequencies of the band pass filter, the series impedance Z_1 is
Option A:	Capacitive at f_1
Option B:	inductive at f_1
Option C:	resistive at f_2
Option D:	zero at f_2
20.	The phase constant β of the filter during stop band is
Option A:	Zero radian
Option B:	2
Option C:	Π
Option D:	2π

Q2	Solve any Two Questions out of Three 10 marks each
A	Define transient period and transient response. The series RC circuit shown in figure, the voltage across C starts increasing when the DC source is switched ON. The rate of increase of voltage across C at the instant just after the switch is closed i.e., at $t = 0^+$ will be –

B	<p>State the steps for solving the example based on Thevenin's theorem. Prove that, at maximum power condition the efficiency is ---%</p>
C	<p>Obtain the dotted equivalent circuit for the coupled circuit shown in fig. below and find mesh currents. Also find the voltage across the capacitor.</p>

Q3.	Solve any Two Questions out of Three 10 marks each
A	<p>Currents I_1 and I_2 entering at port 1 & port 2 respectively of a two-port network are given by following equations: $I_1 = 0.5 V_1 - 0.2 V_2$ $I_2 = -0.2 V_1 + V_2$ Find Y, Z and ABCD parameters for the network.</p>
B	<p>Test whether the polynomial $P(s) = s^7 + 2s^6 + 2s^5 + s^4 + 4s^3 + 8s^2 + 8s + 4$ is Hurwitz</p>
C	<p>What is filter? Find the characteristic impedance, cut-off frequency and pass band for the network shown below.</p>

University of Mumbai
Examination 2021 under Cluster 06
(Lead College: Vidyavardhini's College of Engg Tech)
Examinations Commencing from 15th June 2021

Program: **Electronics Engineering**

Curriculum Scheme: Rev 2016

Examination: SE Semester III

Course Code: ELX305 and Course Name: Electronic Instruments and Measurements

Time: 2 hour

Max. Marks: 80

Q1	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks
Q1.	Strain gauge, LVDT and thermocouple are examples of
Option A:	Storage Devices
Option B:	Filters
Option C:	Transducers
Option D:	Display Units
Q2.	A digital storage oscilloscope has _____ of operation
Option A:	3 primary modes
Option B:	2 primary modes
Option C:	4 primary modes
Option D:	5 primary modes
Q3.	The analog signal is digitized using _____
Option A:	D/A converter
Option B:	Oscillator
Option C:	A/D converter
Option D:	Rectifier
Q4.	Which part is called as heart of CRO?
Option A:	CRT
Option B:	Sweep generator
Option C:	Trigger circuit
Option D:	Amplifier
Q5.	In terms of the division on screen, the voltage of the waveform in CRO is
Option A:	Average voltage
Option B:	RMS voltage
Option C:	Peak to peak voltage
Option D:	Maximum voltage
Q6.	Smallest change which a sensor can detect is _____

Option A:	Resolution
Option B:	Accuracy
Option C:	Precision
Option D:	Scale
Q7.	A rotameter is a device used to measure
Option A:	Velocity of fluid in pipes
Option B:	Velocity of gauges
Option C:	Vortex flow
Option D:	Flow of fluids
Q8.	A type J thermocouple is made of the following metals:
Option A:	Aluminum and Tungsten
Option B:	Iron and Constantan
Option C:	Platinum and Platinum/Rhodium alloy
Option D:	Copper and Constantan
Q9.	Function of transducer is to convert
Option A:	Electrical signal into non electrical quantity
Option B:	Non electrical quantity into electrical signal
Option C:	Electrical signal into mechanical quantity
Option D:	Mechanical to non mechanical quantity
Q10.	Change in output of sensor with change in input is _____
Option A:	Threshold
Option B:	Slew rate
Option C:	Sensitivity
Option D:	Fidelity
Q11	Wheatstone bridge is a _____
Option A:	A.c. bridge
Option B:	D.c. bridge
Option C:	High voltage bridge
Option D:	Power dissipation bridge
Q12.	Sensitivity is defined as _____
Option A:	Amount of voltage per unit current
Option B:	Amount of power per unit voltage
Option C:	Amount of resistance per unit voltage
Option D:	Amount of deflection per unit current
Q13	Kelvin's bridge consists of _____
Option A:	Double bridge
Option B:	Single bridge

Option C:	Half bridge
Option D:	Three fourth bridge
Q14	Closeness of measured value to true value is _____
Option A:	Accuracy
Option B:	Precision
Option C:	Correction
Option D:	Uncertainty
Q15	Which of the following is caused by Careless handling?
Option A:	Systematic error
Option B:	Gross error
Option C:	Random error
Option D:	Non systematic error
Q16	In a measurement, what is the term used to specify the closeness of two or more measurements?
Option A:	Precision
Option B:	Accuracy
Option C:	Fidelity
Option D:	Threshold
Q17	In function generator, the output waveform of integrator is
Option A:	Sinusoidal
Option B:	Square
Option C:	Triangular
Option D:	Saw-tooth
Q18	Vibration galvanometers are used for _____
Option A:	Very high frequency
Option B:	Very low frequency
Option C:	Low audio frequency
Option D:	High audio frequency
Q19	For very small value of resistances we use
Option A:	Maxwells Bridge
Option B:	Wheatstones bridge
Option C:	Kelvins double bridge
Option D:	Megger
Q20	On what Principle does the Q meter operate
Option A:	Series Resonance
Option B:	Parallel Resonance

Option C:	Partial Indication
Option D:	Null Deflection

Q2 (20 marks)	Solve any four out of six	5 marks each
A	How can we minimize errors in Instruments	
B	Explain in detail potentiometric transducer	
C	Explain megger bridge (mega ohmmeter) for high resistance measurement with diagram.	
D	What are Lissajous patterns ? Give its application	
E	Compare sensors and transducers	
F	Explain the operation of spectrum analyzer	

Q3. (20 Marks)	Solve any Four out of Six	5 marks each
A	Compare between CRO and DSO.	
B	Draw the neat diagram and explain the operation of successive Approximation type DVM.	
C	Explain the operation of Electromagnetic flow meter	
D	Explain Fidelity & Dynamic Error	
E	Describe operating principle of heterodyne wave analyzer with a neat block diagram.	
F	Compare RTD, Thermocouple and Thermistor.	