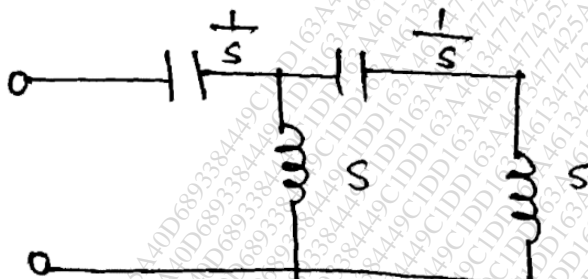


Please check whether you have the right question paper.


- N.B.:**
- 1) Questions No.1 is compulsory.
 - 2) Solve any three questions out of remaining five questions.
 - 3) Figures to the right indicate full marks.

1. a) State and explain properties of positive real function. (05)
- b) Compare series and parallel resonance circuit. (05)
- c) Determine the driving point impedance of the network shown. (05)



- d) Determine whether $p(s) = s^4 + s^3 + 2s^2 + 3s + 2$ is Hurwitz. (05)

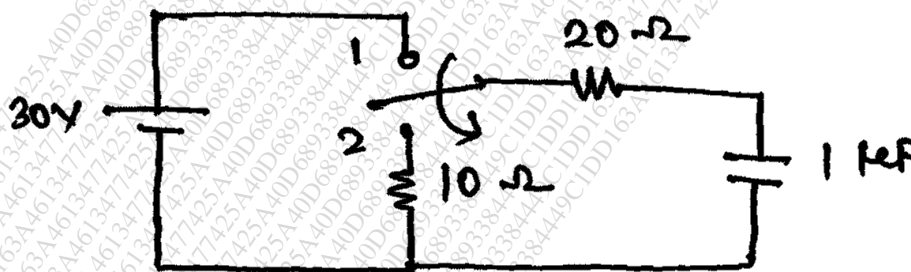
2. a) In the network shown the switch is changed from position 1 to 2 at $t = 0$. Find the values of i , $\frac{di}{dE}$ and $i \cdot \frac{d^2i}{dt^2}$ at $t = 0^+$. (10)



- b) Find the Foster forms of the following impedance function : (10)


$$z(s) = \frac{(s+1)(s+4)}{(s+5)(s+3)}$$

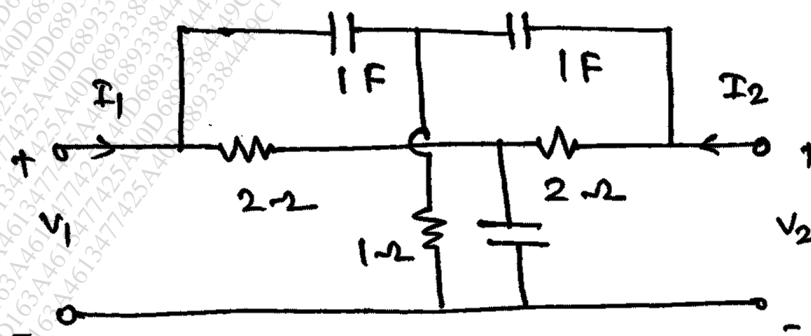3. a) Find Y parameters for the network shown : (10)



TURN OVER

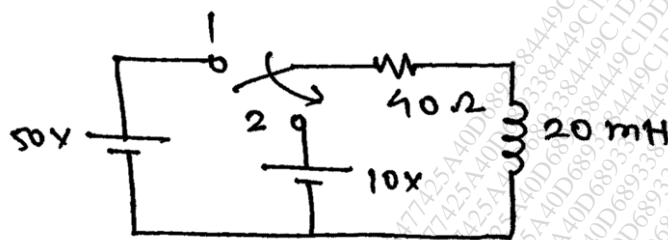- b) The network given below is under steady state with switch at position 1. At $t = 0$ the switch is moved to positions 2. Find $i(t)$. (10)




4. a) Test whether the following function is positive real : (05)


$$f(s) = \frac{s^2 + 6s + 5}{s^2 + 9s + 14}$$

- b) Derive the condition for reciprocity and symmetry for the network in terms of z parameters. (10)
- c) Derive the relation for characteristic impedance of a transmission line. (05)

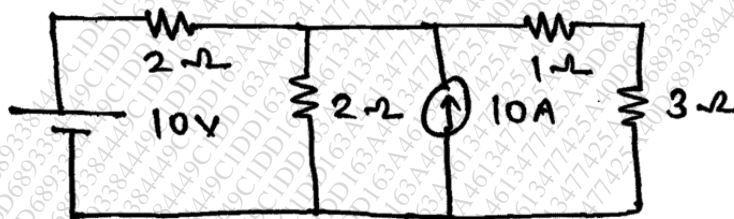
5. a) Find the current through 3Ω resistor using Thevenin's theorem : (05)



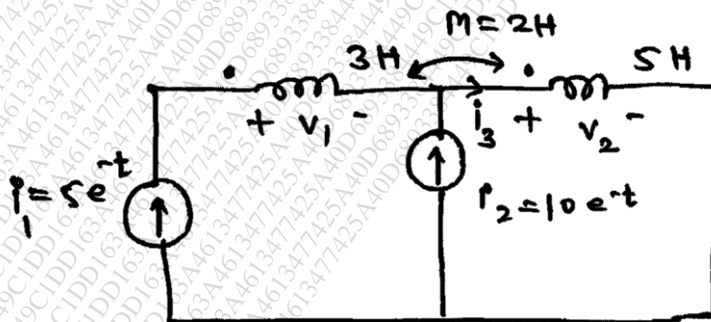- b) In the network shown find the voltages v_1 & v_2 : (05)




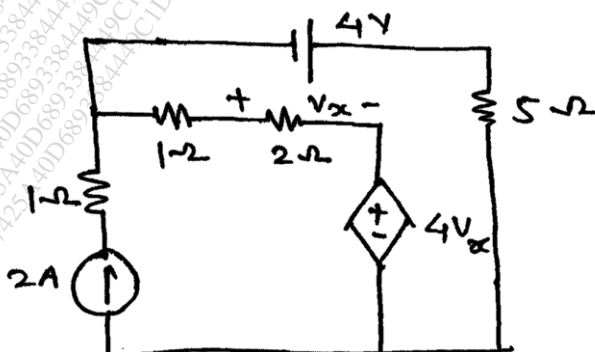- c) Find the current through 5Ω resistor for the network given below : (10)



TURN OVER

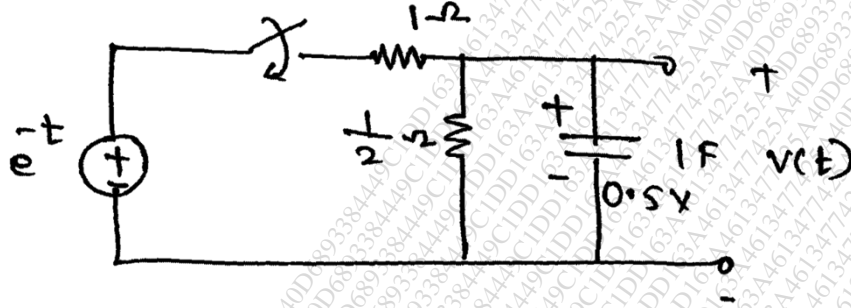6. a) The characteristic impedance of a high frequency line is 100Ω . It is terminated in an impedance of $100 + j100\Omega$. Using a smith chart find the impedance at $\frac{1}{8}$ wavelength away from the load end.
- b) In the network shown the switch is closed at $t = 0$ connecting a source e^{-t} to the network at $t = 0$. $V_c(0) = 0.5 \text{ V}$. Determine $V(t)$.



[Time: 3Hours]

[Marks:80]

- N.B:**
1. Question No. 1 is compulsory.
 2. Out of remaining questions, attempt any THREE questions.
 3. Assume suitable data, wherever necessary.

- Q1 Attempt any Four: 20**
- a) Construct 2-input EX-OR and EX-NOR Gates using only NAND gates.
 - b) Differentiate between Combinational and Sequential Circuits.
 - c) Write truth table and draw logic diagram of Half Adder.
 - d) Explain any five features of VHDL.
 - e) Design MOD-6 counter using IC 7490.

- Q2 a Simplify $F = \sum m (0,2,5,8,10, 12, 15) + d (1,6)$ using K-map. 10**
 Implement the function using only NOR gates.
- b Design 8-bit comparator using four bit magnitude comparator IC 7485. 10**

- Q3 a Design Mod-8 synchronous counter using JK flip-flop. Draw output Waveform. 10**
- b Eliminate the redundant states and draw the reduced state diagram. 10**

PS	NS		O/P
	X=0	X=1	
	B	C	1
A	D	C	0
B	F	E	0
C	E	B	1
D	B	C	1
E	C	E	0
F	C	E	0
G	F	G	0

- Q4 A Implement $F_1 (A, B, C) = \sum m (0,2,4,7)$ 10**
 $F_2 (A, B, C) = \sum m (1,2,5,7)$
 Using IC 74151, 8:1 Multiplexer.

- b Design a mealy sequence detector to detect ----1011-----using D flip-flops, Wherein overlapping is allowed. 10**

- Q5 a List out different types of PLD's. Implement the given functions using PLA. 10**
 $F_1 (A,B,C) = \sum m (3,6, 7)$ $F_2(A,B,C) = \sum m (1,2,4, 7)$

- b Draw neat diagrams of 2-input TTL NAND gate and explain in brief. 10**

- Q6 Write short notes on (any Four) 20**

- a) CPLD Architecture
- b) Stuck at 0 & 1 Faults
- c) Johnson Counter & its applications
- d) State Assignment Techniques
- e) JK-Flip flop

(3 Hours)

(Total Marks : 80)

N.B: (1) Question No.1 is compulsory and solves any three questions from remaining questions.

(2) Assume suitable data if necessary.

(3) Draw neat and clean figures.

1. Answer Any Two :

- a) Compare effect of temperature in BJT, JFET, Diode and MOSFET. **10**
- b) With neat diagram, explain the operation of UJT relaxation oscillator. **10**
- c) Explain construction, working and characteristics of photodiode. **10**

2. a) Explain concept, working and characteristics of Tunnel diode. **10**
- b) Why FET is called as square law device? Differentiate between BJT and FET. **10**

3. a) Determine ideal reverse saturation current density in a silicon PN junction at $T = 300^\circ \text{K}$. Consider the following parameters in a silicon PN junction : $N_a = N_d = 10^{16} \text{ cm}^{-3}$, $n_i = 1.5 \times 10^{10}$, $E_r = 11.7$, $D_p = 10 \text{ cm}^2/\text{S}$, $D_n = 25 \text{ cm}^2/\text{S}$, $\tau_{p0} = \tau_{n0} = 5 \times 10^{-7}$. **10**
- b) Discuss Ebers moll model for BJT in detail. **10**

4. a) Describe construction, working and characteristics of: **10**
- i) DIAC
- ii) IGBT
- b) Draw and explain VI characteristics of Triac **05**
- c) Sketch and explain characteristics of PN junction solar cell **05**

5. a) Justify space charge width increases with reverse bias voltage in a pn junction diode. **10**
- b) Explain the need of heterojunction? Explain the terms straddling, staggered and broken gap in relation to heterojunction **10**

6. Write short notes (Any Three) : **20**

- (a) Optocoupler
- (b) SCR
- (c) Comparison of photodiode and avalanche photodiode
- (d) Comparison of DMOSFET and EMOSFET

(3 Hours)

[Total Marks : 80]

Note:- 1) Question number 1 is compulsory.

2) Attempt any three questions from the remaining five questions

3) Figures to the right indicate full marks.

- Q.1 a) Find the Laplace transform of $\cos t \cos 2t \cos 3t$ 05
- b) Show that the set of functions $\cos nx$, $n=1,2,3,\dots$ is orthogonal over $(0, 2\pi)$ 05
- c) Prove that $f(z) = (x^3 - 3xy^2 + 2xy) + i(3x^2y - x^2 + y^2 - y^3)$ is analytic and find $f'(z)$ 05
in terms of z .
- d) Find the directional derivative of $\phi = x^2 + y^2 + z^2$ in the direction of the line $\frac{x}{3} = \frac{y}{4} = \frac{z}{5}$ 05
at $(1, 2, 3)$
- Q.2 a) Find the fourier series for $f(x) = x^2$ in $(0, 2\pi)$ 06
- b) Show that the vector $\vec{F} = (x^2 + xy^2) \mathbf{i} + (y^2 + x^2y) \mathbf{j}$ is irrotational and find its scalar potential 06
- c) Prove that the transformation $w = \frac{1}{z+i}$ transforms real axis of z - plane into a circle 08
of w - plane
- Q.3 a) Using convolution theorem, find inverse Laplace transform of $\frac{s^2}{(s^2+2)^2}$. 06
- b) Prove that $J_{5/2}(x) = \sqrt{\frac{2}{\pi x}} \left(\frac{3-x^2}{x^2} \sin x - \frac{3}{x} \cos x \right)$ 06
- c) Find half range cosine series for $f(x) = x(\pi - x)$, $0 < x < \pi$. Hence show that $\sum_{n=1}^{\infty} \frac{1}{n^4} = \frac{\pi^4}{90}$ 08

Q.4 a) Evaluate by Green's theorem $\int_c (e^{x^2} - xy) dx - (y^2 - ax)dy$ where c is the circle $x^2 + y^2 = a^2$. 06

b) Prove that $2 J_0''(x) = J_2(x) - J_0(x)$. 06

c) i) Evaluate $\int_0^\infty \frac{e^{-t} - e^{-3t}}{t} dt$ 08

ii) Find Laplace transform of $t \sqrt{1 + \sin t}$

Q.5 a) Find the orthogonal trajectory of the family of curves $x^3y - xy^3 = c$. 06

b) Prove that $\int x \cdot J_{2/3}(x^{3/2}) dx = -\frac{2}{3} x^{-1/2} J_{-1/3}(x^{3/2})$. 06

c) Obtain complex form of Fourier Series for $f(x) = e^{2x}$ in $(0, 2)$. 08

Q.6 a) Use stoke's Theorem to evaluate $\int_C \vec{F} \cdot d\vec{r}$ where $\vec{F} = yz i + zx j + xy k$ and C is the boundary of the circle $x^2 + y^2 + z^2 = 1$ and $z = 0$. 06

b) Find the fourier integral representation for 06

$$f(x) = e^{ax}, x \leq 0, a > 0$$

$$= e^{-ax}, x \geq 0, a > 0$$

Hence show that $\int_0^\infty \frac{\cos wx}{w^2 + a^2} dx = \frac{\pi}{2a} e^{-ax}, x > 0, a > 0$

c) Solve using Laplace transform $(D^2 + 2D + 5)y = e^{-t} \sin t$, where $y(0) = 0, y'(0) = 1$. 08

Duration :3 Hours

Marks:80

- N.B.:** (1) Question No. 1 is compulsory.
 (2) Solve any three questions from remaining five questions.
 (3) Draw neat diagrams and assume suitable data wherever necessary. Justify your assumptions.

Question no 1.**Solve any four**

- Define the following terms:-
Accuracy, Precision, Sensitivity, Linearity and Resolution (5M)
- Draw Venturi meter for flow measurement. (5M)
- Draw and explain the working of practical Q-meter circuit. (5M)
- Write the specification of CRO. (5M)
- Compare digital and analog measuring meters. (5M)

Question no 2. Attempt the following

- Draw and explain the block diagram of CRO .List advantage and disadvantages of it. (10M)
- Draw and explain Kelvin double bridge for measurement of unknown resistance (10M)

Question no 3. Attempt the following

- Draw and explain Maxwell bridge for inductance measurement with expressions involved in it. List drawbacks of it. (10M)
- What are the types of errors in measurement systems? Explain all in details. (10M)

Question no 4. Attempt the following

- Draw and explain ultrasonic type level transducer.
List advantages and disadvantages of it. (10M)
- Draw and explain Dead weight tester (10M)

Question no 5. Attempt the following

- Draw and explain the construction and working of electronics voltmeter using transistors. (10M)
- Draw & explain block diagram of data acquisition system. (10M)

Question no 6. Write short note on the following (20M)

- Data logger
- Magnetic flow meter.
- DSO
- Static and dynamic characteristics of instruments