

[3 Hours]

[Total Marks :-80]


- N.B:** (1) Question No.1 is compulsory.
 (2) Solves any three out of remaining question.
 (3) Assume suitable data if necessary.

1. Any four

- a Draw characteristics of PN junction in thermal equilibrium and explain. 5
- b. Explain the operation of MOSFET as amplifier. 5
- c. Explain construction, working principle and characteristics of Photodiode. 5
- d. Compare HWR, FWR and Bridge rectifier. 5
- e. Compare Zener and avalanche breakdown 5


2.

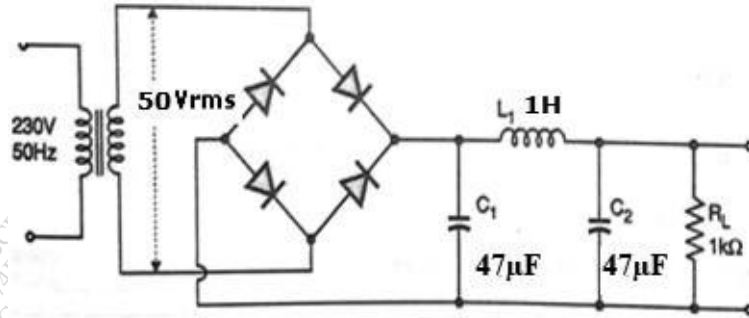- a. Draw and explain positive and negative clamper circuit. 10.
- b. Calculate dc load voltage, an ac ripple in output and ripple factor 10




3.

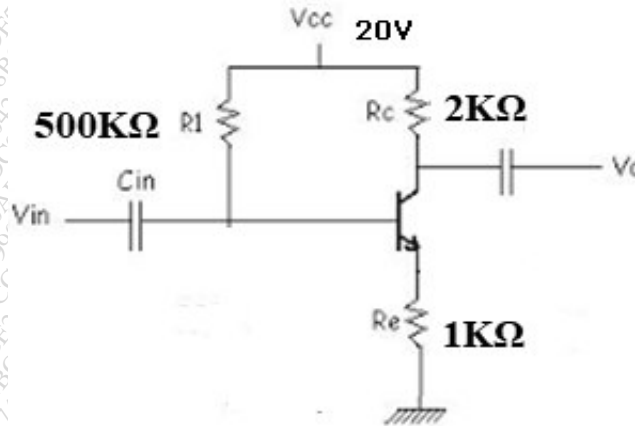- a. Draw and explain VI and CV characteristics of p-channel Enhancement type MOSFET. 10
- b. Find I_B , I_C , V_C , V_E , and V_{CE} for following circuit ($\beta=100$). 10



4

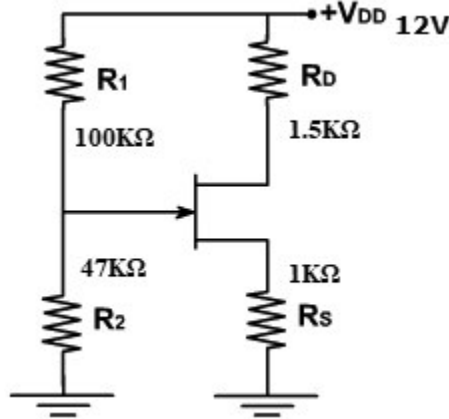- a. Find V_{GSQ} , I_{DQ} , and V_{DSQ} for following circuit. ($V_P = -4V$, $I_{DSS} = 6mA$) 10



- b. Compare CE, CB and CC amplifiers 10


5.

- a. Design single stage CE amplifier for $A_V \geq 110$, $V_{Orms} = 3V$, $h_{FE} = 180$, $h_{fe} = 220$, $h_{ie} = 2.7K\Omega$, $S \leq 10$, $f_L \leq 15Hz$, $V_{CE sat} = 0.25V$, $V_{BE} = 0.7V$. 15

- b) Compare D-MOSFET and E-MOSFET. 05

6

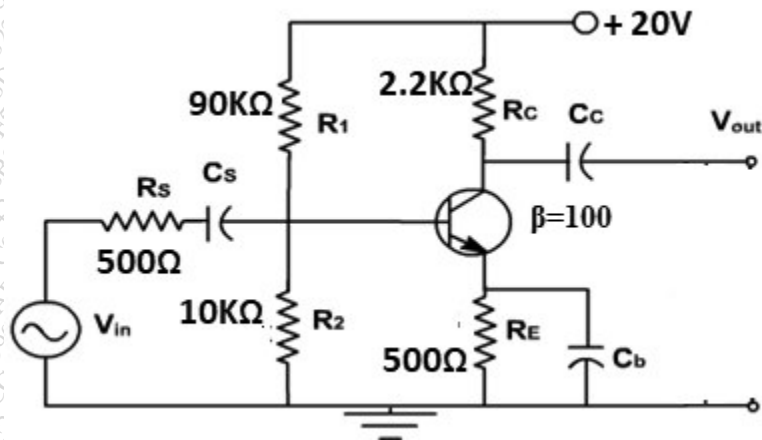- a. Find Z_i , Z_o , A_v and A_{vs} for following circuit. 10



- b) Compare capacitor, inductor, LC and π filter. 10

DBEC DATA SHEET

Transistor type	P _{dmax} @ 25°C Watts	I _{cmax} @ 25°C Amps	V _{ce(sat)} volts d.c.	V _{ce(sat)} volts d.c.	V _{ce(sat)} (S _{us}) volts d.c.	V _{ce(sat)} (S _{us}) volts d.c.	V _{ce(sat)} volts d.c.	V _{ce(sat)} volts d.c.	T _{jmax} °C	D.C. current		Small Signal h _{fe}	h _{fe} max.	V _{as} max.	O _n °C/W 25°C	Derate above 25°C W/°C
										min	typ.					
2N 3055	115-5	15-0	1-1	100	60	70	90	7	200	20	50	50	120	1-8	1-5	0-7
ECN 055	50-0	5-0	1-0	60	50	55	60	5	200	25	50	75	125	1-5	3-5	0-4
ECN 149	30-0	4-0	1-0	50	40	—	—	8	150	30	50	60	115	1-2	4-0	0-3
ECN 100	5-0	0-7	0-6	70	60	65	—	6	200	50	90	280	260	0-9	35	0-05
BC147A	0-25	0-1	0-25	50	45	50	—	6	125	115	180	220	220	0-9	—	—
2N 525(PNP)	0-225	0-5	0-25	85	30	—	—	—	100	35	—	45	—	—	—	—
BC147B	0-25	0-1	0-25	50	45	50	—	6	125	200	290	450	500	0-9	—	—

BFW 11—JFET MUTUAL CHARACTERISTICS

-V _{as} volts	I _{as}		r _d		Derate								
	min	typ	min	typ	above 25°C	above 25°C							
0-0	0-2	0-4	0-6	0-8	1-0	1-2	1-6	2-0	2-4	2-5	3-0	3-5	4-0
10	9-0	8-3	7-6	6-8	6-1	5-4	4-2	3-1	2-2	2-0	1-1	0-5	0-0
I _{as} max. mA	7-0	6-0	5-4	4-6	4-0	3-3	2-7	1-7	0-8	0-2	0-0	0-0	0-0
I _{as} typ. mA	4-0	3-0	2-2	1-6	1-0	0-5	0-0	0-0	0-0	0-0	0-0	0-0	0-0
I _{as} min. mA	—	—	—	—	—	—	—	—	—	—	—	—	—

N-Channel JFET

Type	V _{ds} max. Volts	V _{gs} max. Volts	V _{gs} max. Volts	P _d max. @ 25°C	T _j max.	I _{ass}	I _{ass} (typical)	-V _p Volts	r _d	Derate above 25°C	θ _{ja}
2N3822	50	50	50	300 mW	175°C	2 mA	3000 μU	6	50 KΩ	2 mW/°C	0-59° C/mW
BFW 11 (typical)	30	30	30	300 mW	200°C	7 mA	5600 μU	2-5	50 KΩ	—	0-59° C/mW

DURATION : 3 HOURS

MAX.MARKS:80

- 1) Question No.1 is compulsory
- 2) Attempt any THREE of the remaining
- 3) Figures to the right indicate full marks.

- Q1
- A) Find Laplace transform of $f(t) = \sin^5 t$ 5
- B) Prove that $u = x^2 - y^2$ is harmonic function also find corresponding analytic function $f(z)$ 5
- C) Find the half range sine series of $f(x) = 2x$ in $(0, \pi)$ 5
- D) Find the Unit normal vector to the surfaces $x^2 + y^2 + z^2 = 9$ and $z = x^2 + y^2 - 3$ at $(2, -1, 2)$ hence find angle between them 5
- Q2
- A) Prove that $J_{(-3/2)}(x) = -\sqrt{\frac{2}{\pi x}} \left(\frac{\cos x}{x} + \sin x \right)$ 6
- B) Find the Bilinear transformation which maps the points $z = 1, i, -1$ onto the points $w = 0, 1, \infty$ 6
- C) Obtain the fourier series for $f(x) = x \cos x$ in $(-\pi, \pi)$ 8
- Q3
- A) Find inverse laplace transform of
 (i) $\log\left(\frac{1+s^2}{4+s^2}\right)$ (ii) $\frac{s+5}{(s+4)^3}$ 6
- B) Show that the of functions $\{\cos x, \cos 3x, \cos 5x, \dots\}$ is an orthogonal over $[0, \pi/2]$. Hence construct orthonormal set of functions. 6
- C) Prove that $y = \sqrt{x} \cdot J_n(x)$ is a solution of the equation , 8
- $$x^2 \frac{d^2 y}{dx^2} + (x^2 - n^2 + \frac{1}{4})y = 0$$

Q4

- A) Prove that $\int x^4 J_1(x) dx = x^4 J_2(x) - 2x^3 J_3(x)$ 6
- B) Use Gauss's Divergence theorem to evaluate $\iint_S \bar{N} \cdot \bar{F} ds$ where $\bar{F} = 4xi + 3yj - 2zk$ and S is the surface bounded by $x=0, y=0, z=0$ and $2x + 2y + z = 4$ 6
- C) Solve using Laplace transform $(D^2 + 2D + 1)y = 3te^{-t}$, given $y(0) = -4$ and $y'(0) = 2$ 8

Q5

- A Find Fourier series for 6
- $$f(x) = \begin{cases} \pi + x, & 0 < x < \pi \\ \pi - x, & -\pi < x < 0 \end{cases}$$
- B) Find the image of the region bounded by $x+y=0, x=y, x+y=1, x-y=1$ under the bilinear transformation $w = 2z + 2i$ 6
- c) Prove that $\bar{F} = (y^2 \cos x + z^3)i + (2y \sin x - 4)j + (3xz^2 + 2)k$ is a conservative field 8
- .Find (i) Scalar Potential for \bar{F} (ii) The work done in moving an object in this field from $(0, 1, -1)$ to $(\frac{\pi}{2}, -1, 2)$.

Q6

- A) Find the Laplace Transform of $e^{-t} \int_0^t \sin 3u \cos 2u du$ 6
- B) Find Complex form of Fourier Series of $\sinh 2x$ in $(-2, 2)$ 6
- C) Express the function 8

$f(x) = \begin{cases} 1 & , |x| < 1 \\ 0 & , |x| > 1 \end{cases}$ as Fourier integral .Hence evaluate


$$\int_0^{\infty} \frac{\sin w \cdot \cos wx}{w} dw$$

(3 Hours)


Total Marks: 80

- N.B: (1) Question No. 1 is compulsory.
 (2) Attempt any **three questions** from the remaining.
 (3) Figures to the right indicate full marks.
 (4) Assume suitable data if required.

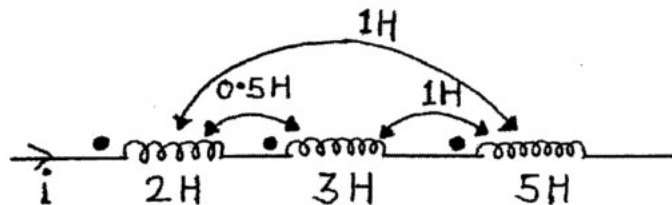- Q.1) (a) Obtain Y parameters in terms of Z parameters. (5)
 (b) Explain the properties of positive real functions. (5)
 (c) Find the equivalent inductance of the network shown. (5)



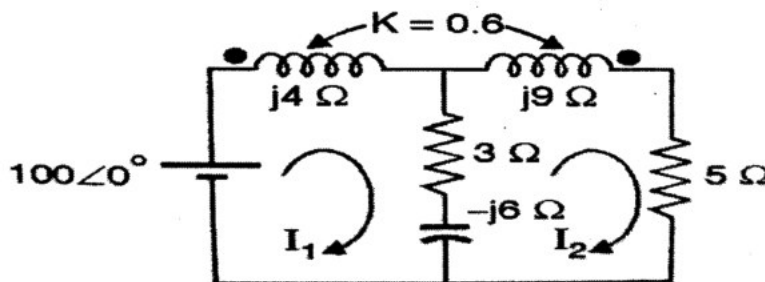- (d) Explain various types of filters (5)
- Q.2) (a) Find currents i_1 and i_2 in the given network using mesh analysis. (10)




- (b) Test whether the following functions are a positive real functions. (10)

(i) $F(S) = \frac{S^4 + 3S^3 + S^2 + S + 2}{S^3 + S^2 + S + 1}$ (ii) $F(S) = \frac{S^2 + 4}{S^3 + 3S^2 + 3S + 1}$

TURN OVER

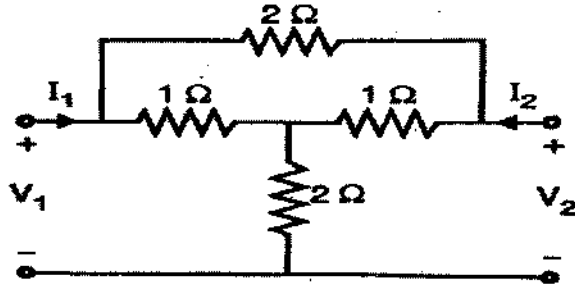Q.3) (a) Determine Y parameter of the interconnected network. (10)




(b) Test whether the following polynomials are Hurwitz polynomials. (10)

(i) $P(s) = s^4 + 5s^3 + 5s^2 + 4s + 10$

(ii) $P(s) = 2s^4 + 5s^3 + 6s^2 + 3s + 1$

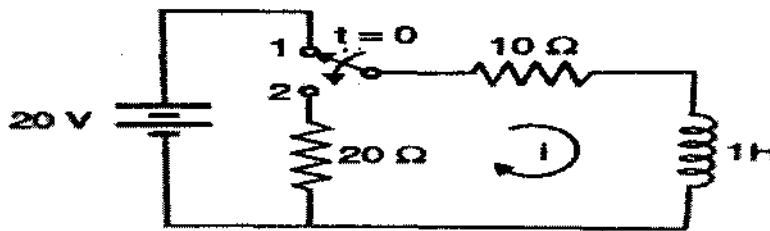
Q. 4) (a) In the circuit given, switch K is changed from position 1 to position 2 at time $t=0$. Find i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at time $t=0^+$. (10)



(b) Determine the Foster forms of realization of the RC impedance function. (10)


$$Z(s) = \frac{(s+1)(s+3)}{s(s+2)(s+4)}$$

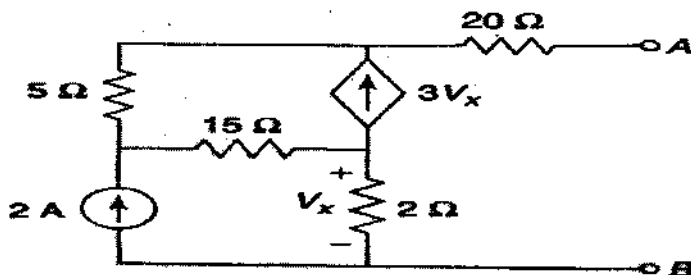Q.5) (a) Find Norton's equivalent of the following network. (10)




TURN OVER

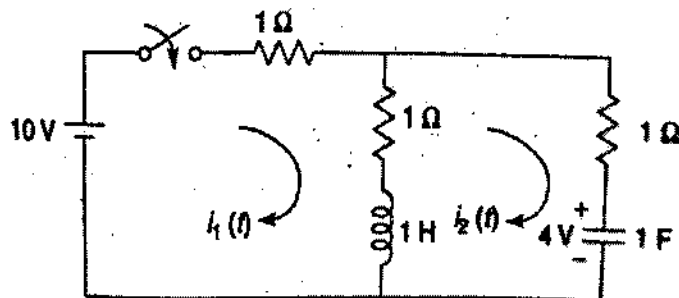
- (b) Find the currents $i_1(t)$ and $i_2(t)$ when initial current through the inductor is zero and initial voltage on the capacitor is 4V. (10)



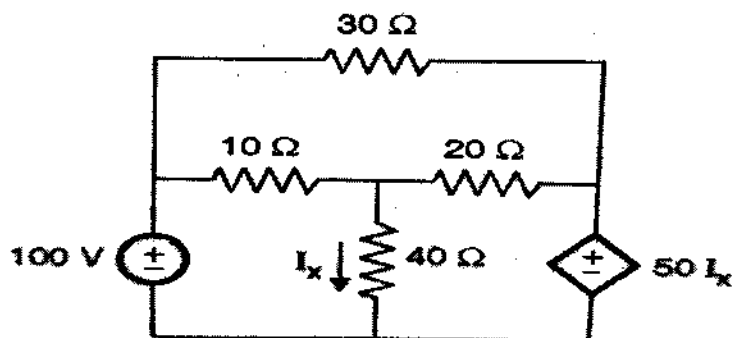
- Q. 6) (a) Find current through 20Ω resistor using mesh analysis. (10)



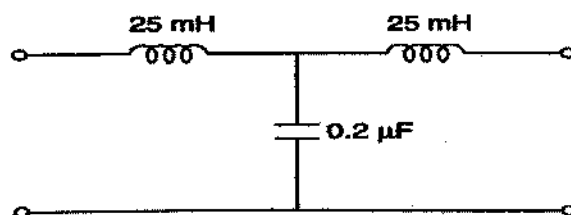- (b) Find the nominal impedance, cut off frequency and pass band for the network. (6)



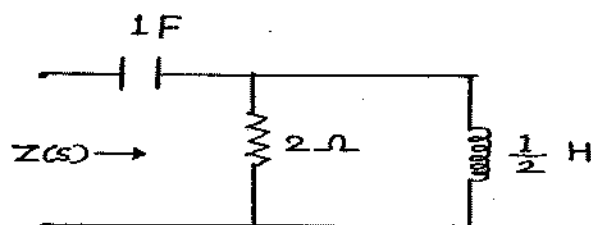- (c) Find poles and Zeros of the impedance of the following network and plot pole zero diagram. (4)



Time: 03Hours

Marks:80 Marks

- (i) Question No. 1 is **compulsory** & attempt any **three** out of the remaining **five** questions.
 (ii) Assume suitable data if required but justify it logically wherever applicable.
 (iii) Figures to the right indicate full marks & every sub-question from Q.2 to Q.6 has equal weightage.

Q. No.	Attempt any four	Marks
Q1.(a)	The expected value of the voltage across a resistor is 80v. However the measurement gives a value of 79v. Calculate (i) absolute error, (ii) % error, (iii) relative accuracy, and (iv) % accuracy.	5
Q1.(b)	Explain Megger Bridge (Mega Ohmmeter) for high resistance measurement with diagram.	5
Q1.(c)	Draw block diagram of Dual trace and dual beam CRO.	5
Q1.(d)	Define Transducers. List selection criteria of Transducers.	5
Q1.(e)	With a neat labelled diagram explain Digital frequency meter.	5
Q1.(f)	List various types of Elastic Pressure Transducers and explain any one.	5
Q2.(a)	What are the different types of errors in measuring instruments? State the remedies to eliminate errors in the measurements.	10
Q2.(b)	Explain the measurement of unknown resistance using Kelvin Double Bridge.	10
Q3.(a)	Explain how Lissajous figures are used for measurements of unknown frequency and phase shift using cathode ray oscilloscope.	10
Q3.(b)	Draw and Explain the block diagram of Digital storage oscilloscope. List any 4 applications of DSO.	10
Q4.(a)	Describe the operation of Successive Approximation type digital voltmeter with a neat block diagram.	10
Q4.(b)	With neat labelled block diagram explain the operation of spectrum analyzer	10
Q5.(a)	Draw and explain construction and working of Linear Variable Differential Transducer and comment on Residual voltage	10

Q5.(b) Draw and explain the construction and working of Dead Weight Tester with labeled diagram. **10**

Q6. (a) Compare RTD, Thermocouple and Thermistor on the basis of the following parameters: **10**

- 1.Principle of working
- 2.Characteristics
- 3.Range
- 4.Applications
- 5.Diagram

Q6.(b) You are asked to measure the flow rate in a network of pipes that carry brine (a salt water solution). At first, it seems an easy task to use electromagnetic flow meters since the brine solution being highly conductive, the output signal obtained is proportional to the flow rate. However, on close inspection, you find that due to several issues: including the storage of space and the myriad of piping the flow transducer and only installed in vertical position. The plant supervisor also tells you “it should be such that” simply by looking at flowrate directly on its scale, he can adjust the valve manually and quickly so as to control it. Which flow transducer will you select for such an application? Explain with a neat diagram. **10**

-----*BEST OF LUCK*-----

Time: 3 Hrs

Marks: 80

- NB:** (1) Question No. 1 is **Compulsory**.
 (2) Attempt any **three** questions out of **remaining five**.
 (3) Each question carries 20 marks and sub-question carry equal marks.
 (4) Assume suitable data if required.

Q.1 Answer Any Four.

- a) Convert the decimal number $(175.23)_{10}$ to their octal, hexadecimal, BCD and gray code equivalent. **5m**
- b) Prove the following Boolean theorem. **5m**
 $(A+\bar{A}B) = (A+B)$
- c) Implement CMOS inverter and NOR gate. **5m**
- d) Design and implement half subtractor circuit. **5m**
- e) Explain various triggering methods and symbols of flip flops. **5m**

- Q.2** a) Simplify the logic function using Quine-McClusky method. **10m**
 $Y(A, B, C, D) = \sum m(0, 1, 2, 3, 5, 7, 8, 9, 11, 14)$
 b) Design and implement D flip flop using T flip flop and JK flip flop using D flip flop. **10m**

- Q.3** a) Design and implement asynchronous MOD-9 counter using T flip flop. **10m**
 b) Draw and explain 5bit comparator using IC 7485. **10m**

- Q.4** a) Implement and explain 4-bit BCD adder using IC 7483. **10m**
 b) Design and implement the following expression using a single 8:1 multiplexer. **10m**
 $Y(A, B, C, D) = \sum m(0, 2, 3, 6, 8, 9, 12, 14)$

- Q.5** a) Draw and explain master slave JK flip flop with its advantage. Derive characteristics equation and excitation table of JK flip-flop. **10m**
 b) Implement and explain 4-bit twisted ring counter. **10m**

- Q.6** Write a short note on **any three**. **20m**
 a) Hamming code
 b) Characteristics of logic families
 c) Static and dynamic Hazards
 d) Application of flip flop in switch debouncing